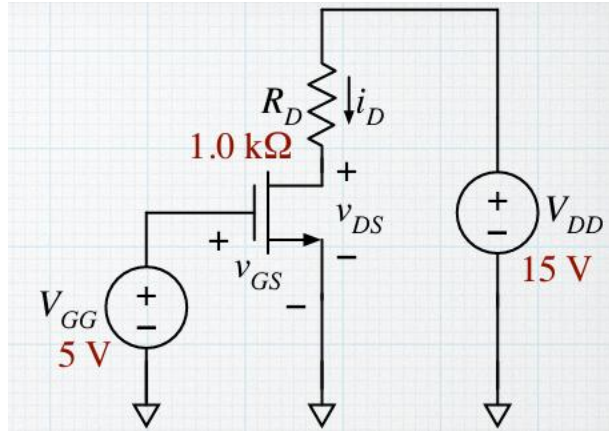



Problem 1: For the circuit below, find the value of i_d and v_{DS} . Assume that the MOSFET threshold voltage is 1V, and $\beta_n = \mu_n C_{ox} \frac{W}{L} = 1 \text{ mA/V}^2$. What region of operation is the NMOS operating in?



Problem 2: Consider a CMOS inverter with the following parameters: $V_{DD}=3\text{V}$, $V_{TN} = 0.6\text{V}$, $V_{TP} = -0.82\text{V}$, $\mu_n C_{ox}=100 \text{ } \mu\text{A/V}^2$, $\mu_p=2.2 \text{ } \mu\text{p}$.

- Determine the β -ratio (β_n / β_p) for a switching threshold of $V_M = 1.3\text{V}$.
- Determine the PMOS device width and length if the NMOS device width is $1 \text{ } \mu\text{m}$ and length is 500nm .

Problem 3: Consider a CMOS inverter as follows, where V_{DD} is 5V, and GND is 0. Assume that there is a sinusoidal voltage at the input, V_{IN} as below, where $V_m=5\text{V}$. Sketch the output voltage V_{OUT} assuming a switching threshold V_M of 2.5V. Clearly show the points where the output voltage transitions.

 

Problem 4: Sketch a 3-input NOR gate with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).