 


Problem 1: Consider a unit sized two-input NOR gate. (5 points)

- Determine the activity factor $\alpha_{0 \rightarrow 1}$ for this gate.
- Calculate the dynamic power consumption of the gate that drives a total $C_{out} = C_{int} + C_L = 12\text{fF}$ capacitance, at 100MHz from a 2V power supply.


Solution:



| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

- From the truth table, $P_1 = \overline{P_A} \cdot \overline{P_B} = 1/4$
 $P_0 = (1 - 1/4) = 3/4$
 $\alpha_{0 \rightarrow 1} = P_0 \cdot P_1 = 3/16 = 0.1875$
- $P_{dyn} = \alpha_{0 \rightarrow 1} C_{out} V_{DD}^2 f = 0.1875 * 12 * 10^{-15} * 2^2 * 100 * 10^6 = 0.9 * 10^{-6} \text{ W} = 0.9 \mu\text{W}$

 Problem 2: Calculate the signal probabilities P_1 , P_2 and activity factors a_1 , a_2 . Here a represents $a_{0 \rightarrow 1}$. The values of P_x, P_y and P_z are given in the figure as $\frac{1}{4}$, $\frac{3}{4}$ and $\frac{1}{2}$. (4 points)



Solution:

$$P_x = \frac{1}{4}, \text{ that makes } \overline{P_x} = \left(1 - \frac{1}{4}\right) = \frac{3}{4}$$

$$\text{Similarly, } \overline{P_y} = \left(1 - \frac{3}{4}\right) = \frac{1}{4}$$

From the NOR truth table from Problem 1 solution, we find

$$P_1 = \overline{P_x} \cdot \overline{P_y} = \left(\frac{3}{4}\right) \cdot \left(\frac{1}{4}\right) = \frac{3}{16} = 0.1875$$

$$\overline{P_1} = \left(1 - \frac{3}{16}\right) = \frac{13}{16}$$

$$a_1 = \overline{P_1} \cdot P_1 = \frac{39}{256} = 0.1523$$

Now let's see a NAND truth table.



$$Q = A \text{ NAND } B$$

Truth Table

| Input A | Input B | Output Q |
|---------|---------|----------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

From the truth table, we see that $\overline{P_2} = P_1 \cdot P_2 = \left(\frac{3}{16}\right) \cdot \left(\frac{1}{2}\right) = \frac{3}{32}$


That makes $P_2 = 1 - \overline{P_2} = 1 - \frac{3}{32} = \frac{29}{32} = 0.9063$

$$a_2 = \overline{P_2} \cdot P_2 = \frac{87}{1024} = 0.085$$


Problem 3: Sketch pseudo-nMOS 3-input NAND and NOR gates. Label the transistor widths so that it is equivalent to the pseudo-nMOS inverter shown in Lecture 7, slide 8. What are the rising, falling, and average logical efforts of each gate? (6 points)

Solution:

NAND3

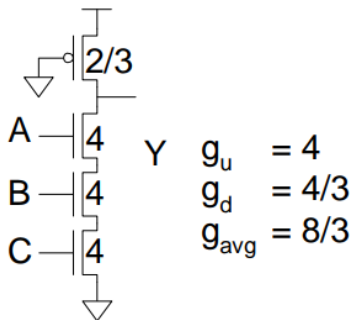

NOR3

 


The inverter has nMOS aspect ratio of 4/3, pMOS aspect ratio of 2/3. For both gates, pMOS aspect ratio remain the same. For nMOS aspect ratio, the calculation is following:

For NAND3:

$R/k + R/k + R/k = R/(4/3)$, we get $k=4$.

 To calculate g_u : we need to make an equivalent unskewed inverter with pMOS aspect ratio 2/3.




$$C_{in} = 4, C_{inv} = (1/3 + 2/3) = 1$$

$$g_u = C_{in}/C_{inv} = 4$$

To calculate g_d : we need to calculate the current through nMOS, and then make an equivalent unskewed inverter.

$$\text{Current through nMOS} = 4I/3 - I/3 = I$$

 So, the equivalent unskewed inverter looks like following:



$$g_u = C_{in}/C_{inv} = 4/3$$

$$g_{avg} = 8/3$$

For NOR3:

$$R/k = R/(4/3), \text{ we get } k=4/3$$

Using the same process as the NAND gate, $g_u = 4/3$, $g_d = 4/9$, $g_{avg} = 8/9$

Problem 4: Design a 4-input footed dynamic NAND gate driving an electrical effort of 1. Estimate the worst charge-sharing noise as a fraction of VDD assuming that diffusion capacitance on uncontacted nodes is about half of gate capacitance and on contacted nodes it equals gate capacitance. (5 points)

Solution: The worst case is when A is low on one cycle, B, C, and D are high, and all the internal nodes become precharged to 0. Then D falls low during precharge. Then A goes high during evaluation. The NAND has 11 units of capacitance on C_{out} precharged to VDD and 7.5 units of internal capacitance (C_1, C_2, C_3) that will be initially low. The output will thus drop to $11/(11+7.5) VDD = 0.59 VDD$.

