

EE 431: COMPUTER-AIDED DESIGN OF VLSI DEVICES

Datapath Functional Units

Nishith N. Chakraborty

November, 2024

OUTLINE




- Comparators
- Shifters
- Multi-input Adders
- Multipliers

COMPARATORS

- 0's detector: $A = 00...000$
- 1's detector: $A = 11...111$
- Equality comparator: $A = B$
- Magnitude comparator: $A < B$


1'S & 0'S DETECTORS

   - 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)




EQUALITY COMPARATOR

 - Check if each bit is equal (XNOR, aka equality gate)
- 1's detect on bitwise equality



MAGNITUDE COMPARATOR

- Compute $B-A$ and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit

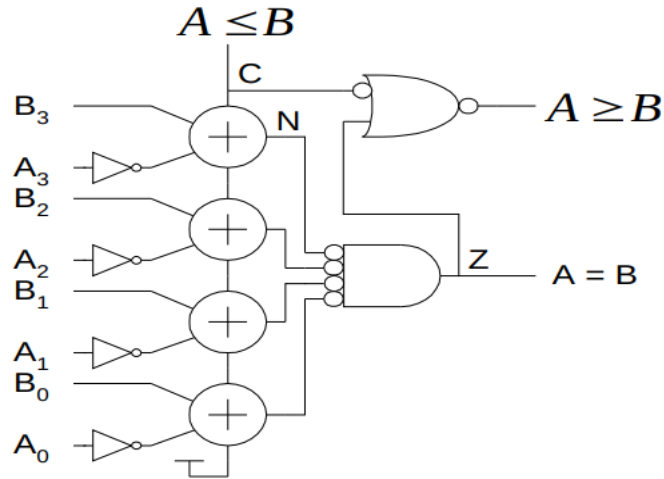

SIGNED VS. UNSIGNED

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)

Table 10.4 Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\overline{Z}	\overline{Z}
$A < B$	$\overline{C} + \overline{Z}$	$\overline{(N \oplus V)} + \overline{Z}$
$A > B$	\overline{C}	$(N \oplus V)$
$A \leq B$	C	$\overline{(N \oplus V)}$
$A \geq B$	$\overline{C} + Z$	$(N \oplus V) + Z$

SHIFTERS


- Logical Shift:
 - Shifts number left or right and fills with 0's
 - $1011 \text{ LSR } 1 = \underline{\hspace{1cm}}$ $1011 \text{ LSL } 1 = \underline{\hspace{1cm}}$
- Arithmetic Shift:
 - Shifts number left or right. Right shift sign extends
 - $11011 \text{ ASR } 1 = \underline{\hspace{1cm}}$ $1011 \text{ ASL } 1 = \underline{\hspace{1cm}}$
- Rotate:
 - Shifts number left or right and fills with lost bits
 - $1011 \text{ ROR } 1 = \underline{\hspace{1cm}}$ $1011 \text{ ROL } 1 = \underline{\hspace{1cm}}$

SHIFTERS

- Logical Shift:
 - Shifts number left or right and fills with 0's
 - $1011 \text{ LSR } 1 = 0101$ $1011 \text{ LSL } 1 = 0110$
- Arithmetic Shift:
 - Shifts number left or right. Right shift sign extends
 - $1011 \text{ ASR } 1 = 1101$ $1011 \text{ ASL } 1 = 0110$
- Rotate:
 - Shifts number left or right and fills with lost bits
 - $1011 \text{ ROR } 1 = 1101$ $1011 \text{ ROL } 1 = 0111$

FUNNEL SHIFTER

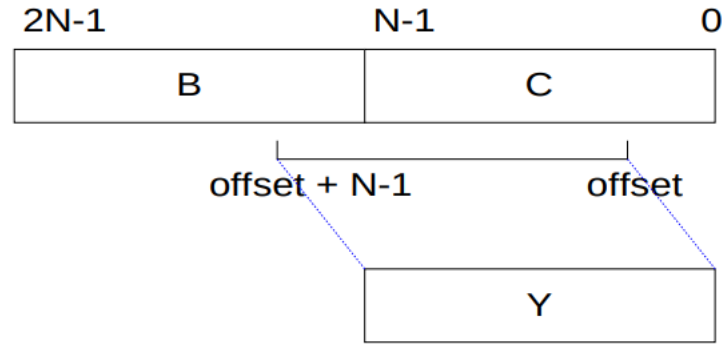- A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



FUNNEL SHIFTER OPERATION

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right			
Arithmetic Left			
Rotate Right			
Rotate Left			

- Computing $N-k$ requires an adder

FUNNEL SHIFTER OPERATION

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left			
Rotate Right			
Rotate Left			

- Computing $N-k$ requires an adder

FUNNEL SHIFTER OPERATION

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right			
Rotate Left			

- Computing $N-k$ requires an adder

FUNNEL SHIFTER OPERATION

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left			

- Computing $N-k$ requires an adder

FUNNEL SHIFTER OPERATION

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	$N-k$

- Computing $N-k$ requires an adder

SIMPLIFIED SHIFTER OPERATION

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0, 0..0$	\overline{k}
Arithmetic Right		
Arithmetic Left		
Rotate Right		
Rotate Left		

SIMPLIFIED SHIFTER OPERATION

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0, 0..0$	\overline{k}
Arithmetic Right	$A_{N-1} \dots A_{N-1}, A_{N-1} \dots A_0$	k
Arithmetic Left		
Rotate Right		
Rotate Left		

SIMPLIFIED SHIFTER OPERATION

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}...A_0$	k
Logical Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Arithmetic Right	$A_{N-1}...A_{N-1}, A_{N-1}...A_0$	k
Arithmetic Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Rotate Right		
Rotate Left		

SIMPLIFIED SHIFTER OPERATION

- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}...A_0$	k
Logical Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Arithmetic Right	$A_{N-1}...A_{N-1}, A_{N-1}...A_0$	k
Arithmetic Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Rotate Right	$A_{N-2}...A_0, A_{N-1}...A_0$	k
Rotate Left		

SIMPLIFIED SHIFTER OPERATION



- Optimize down to $2N-1$ bit input

Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}...A_0$	k
Logical Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Arithmetic Right	$A_{N-1}...A_{N-1}, A_{N-1}...A_0$	k
Arithmetic Left	$A_{N-1}...A_0, 0..0$	\overline{k}
Rotate Right	$A_{N-2}...A_0, A_{N-1}...A_0$	k
Rotate Left	$A_{N-1}...A_0, A_{N-1}..A_1$	\overline{k}


FUNNEL SHIFTER DESIGN 1

  - N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (V_t drops!)



FUNNEL SHIFTER DESIGN 2

 - Log N stages of 2-input muxes
- No select decoding needed



MULTI-INPUT ADDERS


- Suppose we want to add k N -bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = \underline{\hspace{2cm}}$

MULTI-INPUT ADDERS

- Suppose we want to add k N -bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$


MULTI-INPUT ADDERS

 - Suppose we want to add k N -bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- Straightforward solution: $k-1$ N -input CPAs
 - Large and slow




CARRY-SAVE ADDITION (CSA)

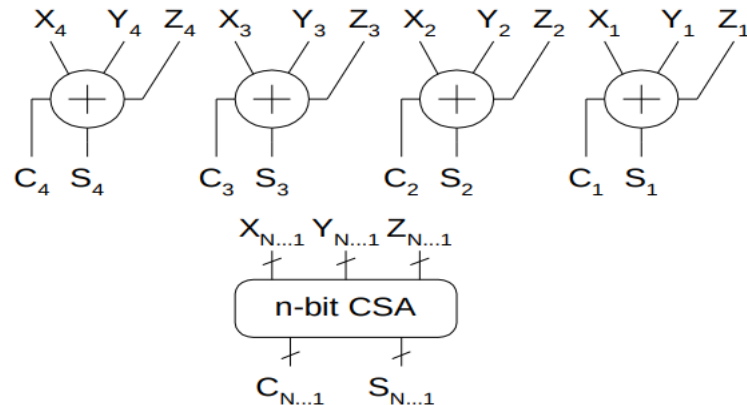- A full adder sums 3 inputs and produces 2 outputs
 - Carry output has twice weight of sum output
- N full adders in parallel are called carry save adder
 - Produce N sums and N carry outs




CSA APPLICATION

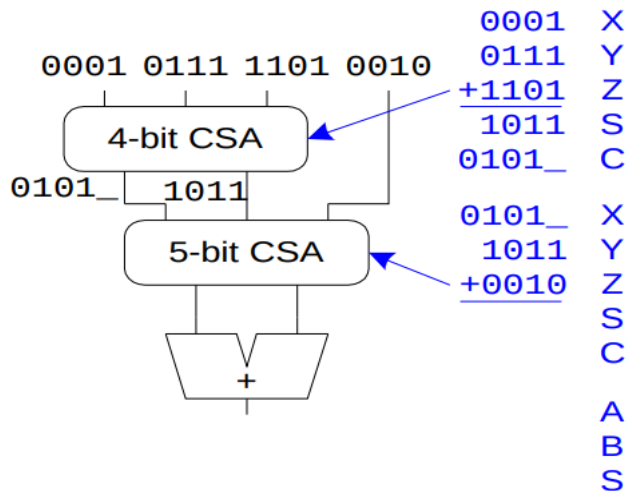- Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result




CSA APPLICATION

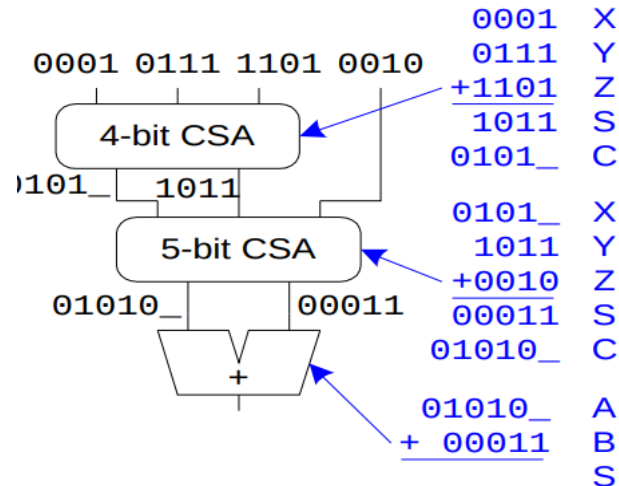- Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result



CSA APPLICATION

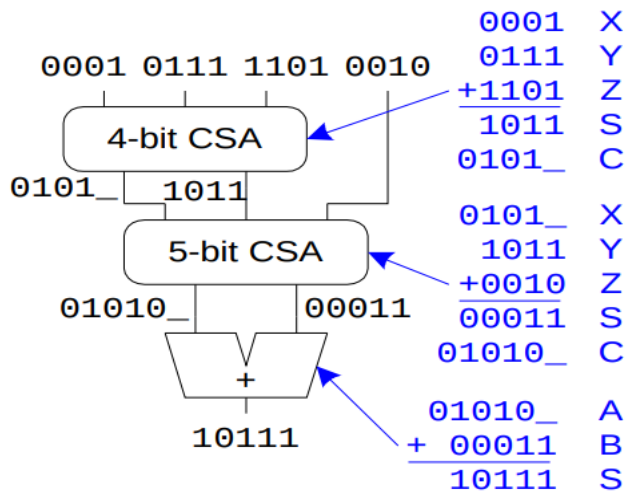- Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result



MULTIPLICATION

- Example:
$$\begin{array}{rcl} 1100 & : & 12_{10} \\ \underline{0101} & : & 5_{10} \end{array}$$

MULTIPLICATION

- Example:

$$\begin{array}{r} 1100 \\ 0101 \\ \hline 1100 \end{array} : \begin{array}{l} 12_{10} \\ 5_{10} \end{array}$$

MULTIPLICATION

- Example:

1100	:	12	₁₀
0101	:	5	₁₀
1100			
0000			

MULTIPLICATION

- Example:

$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 \hline
 \end{array}$$

MULTIPLICATION

- Example:

$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 \end{array}$$

MULTIPLICATION

- Example:

$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 00111100 : 60_{10}
 \end{array}$$

MULTIPLICATION

- Example:

1100	:	12 ₁₀	multiplicand
0101	:	5 ₁₀	
<hr/>			
1100			partial products
0000			
1100			
0000			
<hr/>			
00111100	:	60 ₁₀	product

- M x N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product

GENERAL FORM

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

						y_5	y_4	y_3	y_2	y_1	y_0	
						x_5	x_4	x_3	x_2	x_1	x_0	
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$				
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$					
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$						
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	


multiplicand
multiplier

partial
products


product

DOT DIAGRAM

- Each dot represents a bit

 


ARRAY MULTIPLIER

 

RECTANGULAR ARRAY

 - Squash array to fit rectangular floorplan



FEWER PARTIAL PRODUCTS

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products.
 - Faster and smaller?
 - Called radix- 2^r encoding
- Ex: $r = 2$: look at pairs of bits
 - Form partial products of $0, Y, 2Y, 3Y$
 - First three are easy, but $3Y$ requires adder

BOOTH ENCODING


- Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Table 10.12 Radix-4 modified Booth encoding values

Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	X_i	$2X_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	$-0 (= 0)$	0	0	1


BOOTH ENCODING EXAMPLE

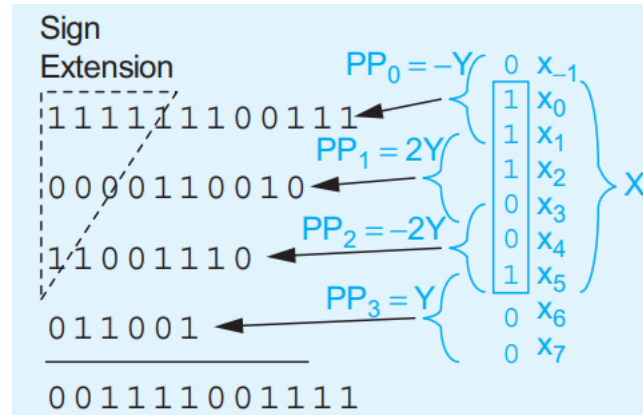- Do the multiplication of $P = Y \times X = 011001_2 \times 100111_2$, applying Booth encoding to reduce the number of partial products.




BOOTH HARDWARE

 - Booth encoder generates control lines for each PP
 - Booth selectors choose PP bits



SIGN EXTENSION

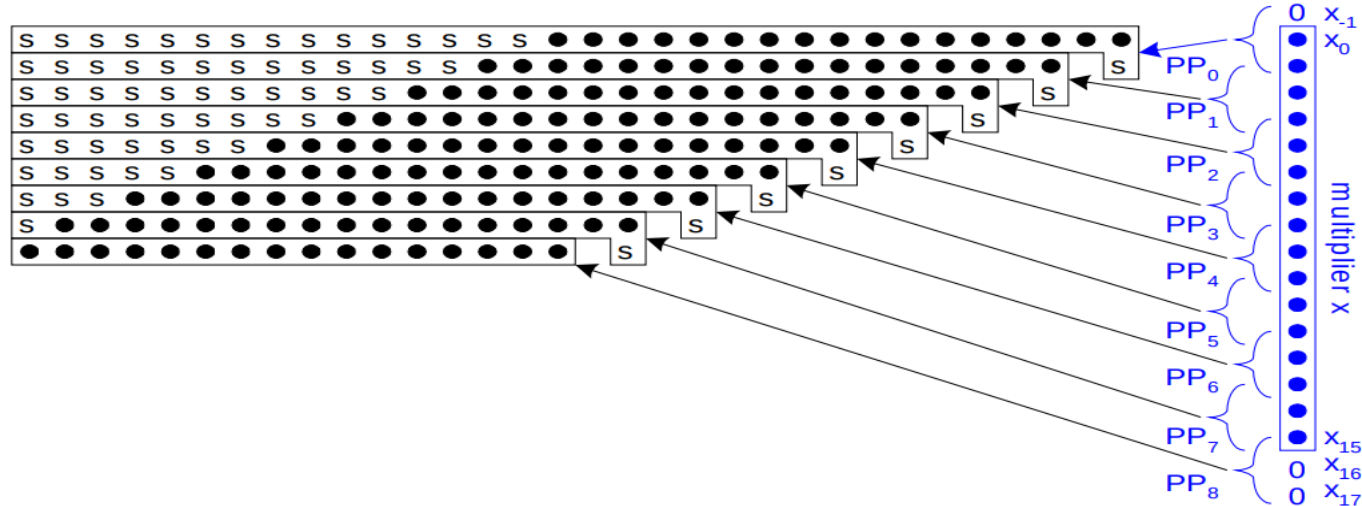- Partial products can be negative
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit



Thank you!