

---

# Lecture 11

## Basic Building Blocks, Revisited

Adapted from: Mark Horowitz  
Stanford University

# Overview

---

- Reading

+ W H 10.2

Addition

- Introduction

We now have all the tools we need to build a chip. We can write Verilog, create test benches, and then synthesize it to make it work. At the start of this class we talked about the basic building blocks for all VLSI: MOS transistors and wires. Now we want to look at the basic building blocks again, but at a higher level. When thinking about higher-level hardware design, what are the common motifs that we use? What does VLSI do well; how should we think about our problem?

# What Makes A Good VLSI Block?

---


Does something useful and is:

- Low power
  - Short wires
- Low area
  - Few wires
- Good performance
  - Short critical paths
- Has nice abstraction
 
# Best Case Density, Design Time – 2D Array

---


- Few wires (or short wires), lots of devices



 
## Good Case – 1D Array

---


- Replicated structure in one direction
  - Usually the bits in a word
- In the other direction you generally have different functions
  - Communication between function units is well defined
  - Mostly communication is between bits in same “slice”



# Datapaths

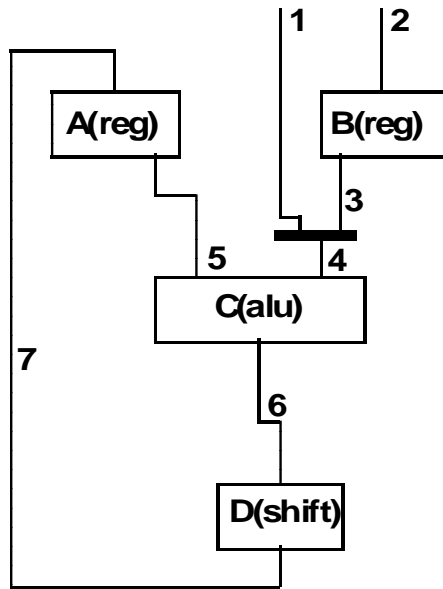

 if all busses are 32 bits  
this is a nightmare to  
interconnect (note: ALU  
inputs need to be  
interleaved)




# Implementing Datapaths / Arrays

---

- Datapaths? Arrays?
  - What does this have to do with my Verilog
  - I am just going to synthesize / place and route design
- For 2-D arrays
  - Certain structures (memories) come as larger blocks
    - Built using a different methodology
  - If you are creating an array of larger blocks
    - Create a separate cell in Verilog hierarchy
    - Then think of arraying that cell in your implementation
- For datapaths
  - Again create a separate file for the datapath
  - Possibly use a different placer for this section

# Memories Have Very Regular Wiring

 

- It has  $N^2$  elements and only  $2N$  wires. Since it is the wires that occupy the most space, these structures are very dense. It is an easy way to use millions of transistors. The layout is quite dense.



# What Do Chips Do?

---

- Mostly move data around
  - Sometimes data must be duplicated
  - Memories are good communication boxes
    - Anyone can store a valid word
    - Someone else can read it later to use it
- Pack and unpack data
  - Extracting headers from packets
  - Extracting byte chars, from words
- Operate on it
  - Arithmetic (+, \*, /) in various types of number systems

# What Do Chips Do, cont'd

## Sequence and Control Stuff

---

- Need to control the part of machine moving data
  - Need to make sure it gets to the right place
  - At the right time
- Can need to coordinate with communication channels
- Or even the user

# What is Data?

---

- Data is always encoded as a binary string
  - Chips only work on bits
- What does that binary string represent?
  - Elements of a set
    - Enumerated types, or presence of members
  - Characters (really an element of a set)
  - Numbers

# Numbers

---

- Numbers are represented by N-bit binary strings.
  - N is chosen to minimize hardware/storage
    - And still get the right answer
- Programs generally use N=32 or 64
  - Hardware uses all different sizes
  - Modern computers have “vector” instructions
    - That allow subword operations(8bit, 16bit)

Numbers come in two forms:

- Fixed Point (Integer), and Floating Point (Real)

# Fixed Point (a.k.a. Integer)

---

- There are two forms of fixed point, signed and unsigned
  - Difference is whether there is a sign bit
- Unsigned
  - Numbers range from 0 to  $2^n - 1$
- Signed
  - Numbers are in two's complement form
  - Range from  $-2^{n-1}$  to  $2^{n-1} - 1$
  - -1 is 11...11 (it is 0 -1)
- The binary point need not be at the end of the number
  - XXX.XXXXX, and this can be signed or unsigned

# Fixed Point Numbers


---

- For fixed point numbers
  - The position of the binary point is not stored
  - The designer of the hardware needs to know this information
- For addition
  - Need to shift numbers to align the binary points
- For multiplication
  - Need to calculate where the binary point is in the product
  - And create the correct product
- Often used in signal processing applications
  - Where the input data has low resolution (images, sensors)
 
# Floating-Point Numbers

---

- Floating Point
  - Even more complicated, contains an exponent field and a mantissa, which give it even more dynamic range.
- IEEE Format Single-Precision Floating-Point numbers:
  - Contain Sign bit, exponent, and mantissa
  - Number represents  $(-1)^S \cdot (1.\text{mantissa}) \cdot (2)^{\text{Exp}-127}$
  - Numbers are in sign magnitude form



# Floating Point Numbers

---

- Current IEEE approved formats:

| Name      | Common name         | Base | Digits | E min  | E max  |
|-----------|---------------------|------|--------|--------|--------|
| binary16  | Half precision      | 2    | 10+1   | -14    | +15    |
| binary32  | Single precision    | 2    | 23+1   | -126   | +127   |
| binary64  | Double precision    | 2    | 52+1   | -1022  | +1023  |
| binary128 | Quadruple precision | 2    | 112+1  | -16382 | +16383 |

- Addition
  - Need to align numbers, then add
    - And if the add was really a subtract, need to renormalize
- Multiplication
  - Need to compute the new exponent



# FP Operation

---

- Adder
- Multiplier

# Other Operations - Shift


---

There are many different kinds of shifters.

- Simple Shifter
  - Shift the number to the right or left and fill-in with zeros
- Arithmetic Shifter
  - Left shifts are the same as simple shifter, but on right shifts use the sign bit to fill-in the new blank spaces (-2 shifted right by 1 gives -1)
    - Need to be careful about arithmetic right shifts. '1' right shifted by 1 is 0. '-1' right shifted by 1 is -1
- Barrel Shifter
  - Wrap the number onto a circle. The shift amount indicates where the new MSB will be. (Useful for rotating the bytes in a 32-bit word)

# Funnel Shifter

---

 

Is the most general kind of shifter

- Concatenates two n-bit words together
  - Then selects any contiguous n-bit subfield
- Can implement all other shifters
  - If A=B get a barrel shifter
  - If A = sign bit, get arithmetic shifts
  - And it does byte inserts too.


# Building a Shifter Using Switch Logic

---

- Each output is really just a large mux
  - Has a nice layout too.
 
# A Mux Based Shifter

- Simplest shifter is 5 stages of 2:1 muxes (32 bit shift)
- Binary shift amount is used as the control signals




# Look Quickly At Addition & Multiplication

---

- Both can be synthesized for you
  - And the results are going to be good
- But both implementation use tricks that are good to know
  - And can be used in other functions you might need
  - And these might not be as easy to automatically synthesize
- Adder's problem
  - Long sequential dependency (carry in to carry out)
  - We will convert linear delay to log delay using trees
- Multiplier's problem
  - Similar, but also needs to compute many adds
 
# Adder Basic Building Block: Full Adder


- Full adder adds three 1-bit numbers
- Inputs are A, B, and C
- Four possible output values: 0,1,2,3 -> coded on two bits
  - Carry is the MSB
  - Sum is the LSB



| a | b | c | Carry | Sum |
|---|---|---|-------|-----|
| 0 | 0 | 0 | 0     | 0   |
| 0 | 0 | 1 | 0     | 1   |
| 0 | 1 | 0 | 0     | 1   |
| 0 | 1 | 1 | 1     | 0   |
| 1 | 0 | 0 | 0     | 1   |
| 1 | 0 | 1 | 1     | 0   |
| 1 | 1 | 0 | 1     | 0   |
| 1 | 1 | 1 | 1     | 1   |
 
# Logical Expressions for Full Adder

- $\text{Carry} = AB + AC + BC$
- $\text{Sum} = A \oplus B \oplus C = A \sim B \sim C + \sim A B \sim C + \sim A \sim B C + A B C$




| a | b | c | Carry | Sum |
|---|---|---|-------|-----|
| 0 | 0 | 0 | 0     | 0   |
| 0 | 0 | 1 | 0     | 1   |
| 0 | 1 | 0 | 0     | 1   |
| 0 | 1 | 1 | 1     | 0   |
| 1 | 0 | 0 | 0     | 1   |
| 1 | 0 | 1 | 1     | 0   |
| 1 | 1 | 0 | 1     | 0   |
| 1 | 1 | 1 | 1     | 1   |


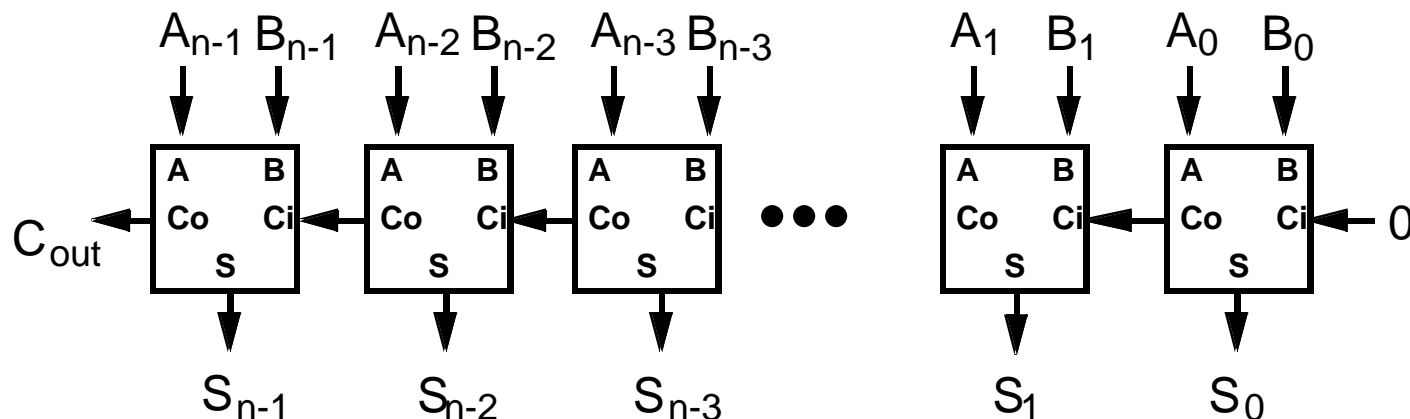
# What Makes Adding Interesting: Adding N-bit Numbers

- Cascade N 1-bit full adders together
  - Two N-bit numbers connected to A and B inputs
  - C ( $C_i$ ) and Carry ( $Co$ ) inputs connected in a daisy chain
  - Set first  $C_i$  to be 0
  - Last  $Co$  indicates overflow
- Known as a Ripple Carry Adder (delay proportional to N)
  - It is used (good for small N)



# Fast Adders

---

- Need to remove the linear dependency chain
  - Or make it much shorter
- How?
  - Need to do calculation in parallel
- But how, we have sequential dependency chain
  - Leverage that the equations for  $C_{in}$  are associative
  - Thus they can be done in any order
- Easiest seen by defining
  - PGK

# PGK

---

- For a full adder, define what happens to Cout
  - Generate:  $C_{out} = 1$  independent of C
    - $G = A \cdot B$
  - Propagate:  $C_{out} = C$ 
    - $P = A \oplus B$
  - Kill:  $C_{out} = 0$  independent of C
    - $K = \sim A \cdot \sim B$

# Using Generate / Propagate


---

- $C_i = G_i + P_i C_{i-1}$ 
  - Note you can use  $P = A+B$  here, why?
- $C_{i+1} = G_{i+1} + P_{i+1} C_i = G_{i+1} + P_{i+1} G_i + P_{i+1} P_i C_{i-1}$ 


Group the terms in the above expression and name them as:

$$G_{i+1;i} = G_{i+1} + P_{i+1} G_i$$
$$P_{i+1;i} = P_{i+1} P_i$$
- Generate and propagate for groups spanning  $i:j$ 
  - i.e.,  $G_{i;j}$  (for  $i > j$ ) =  $G_{i;k} + P_{i;k} G_{k-1;j}$  (for  $i \geq k > j$ )
  - i.e.,  $P_{i;j}$  (for  $i > j$ ) =  $P_{i;k} P_{k-1;j}$  (for  $i \geq k > j$ )
- Sum:  $S_i = P_i \text{ XOR } G_{i-1;0}$

# PG Logic

 


# Carry-Ripple Revisited

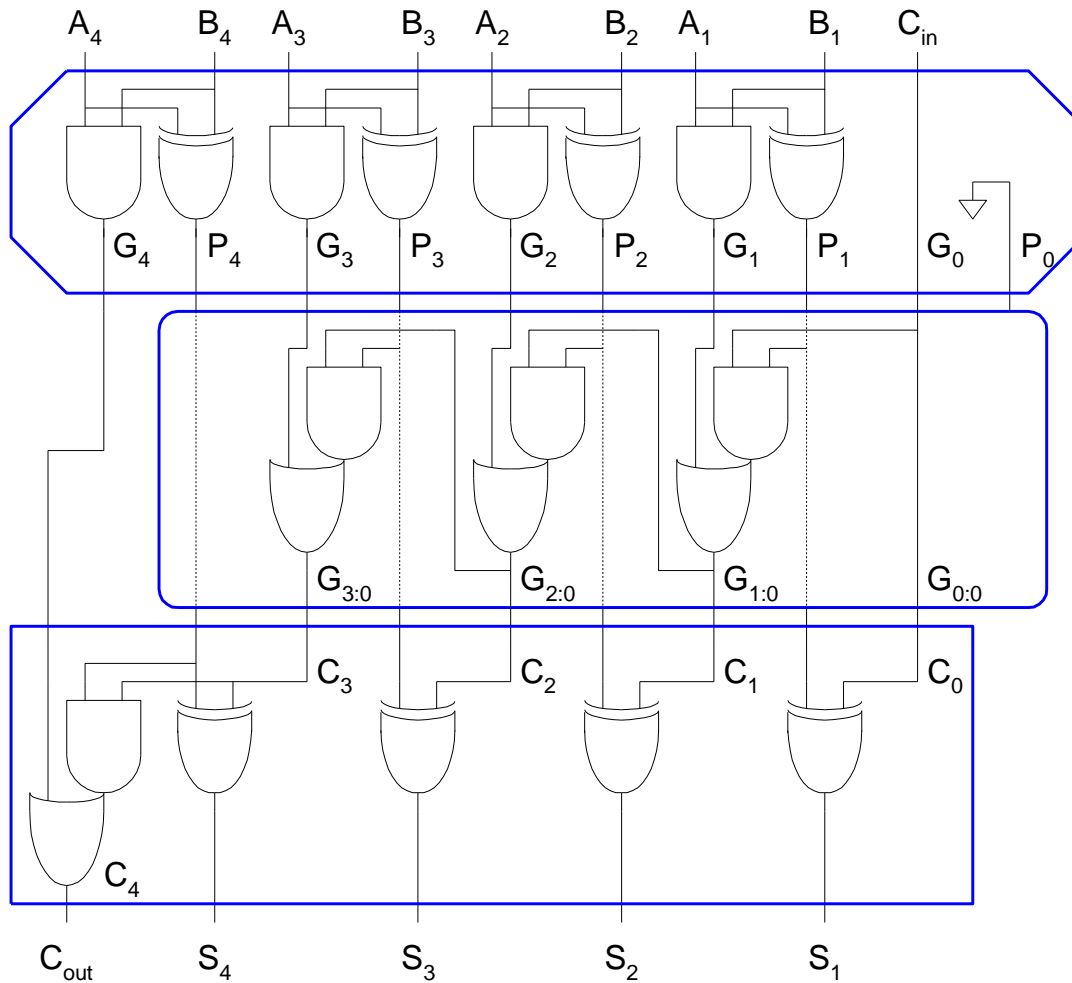


# PG Diagram Notation





Black cell

 

Gray cell

 


Buffer

    
 
# Carry-Ripple PG Diagram

$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{\text{xor}}$$

- Carry-ripple is slow through all N stages






# Tree Adder


---

- The P and G for the group computation is associative
  - Means you can compute the groups in any order
- Like a large fanin and gate
  - You can create a tree to compute the needed output
  - And the terms you create can be reused
  - The resulting delay is logarithmic with N
- Many variations on tree adders
  - Different ways reusing the outputs


# Sklansky

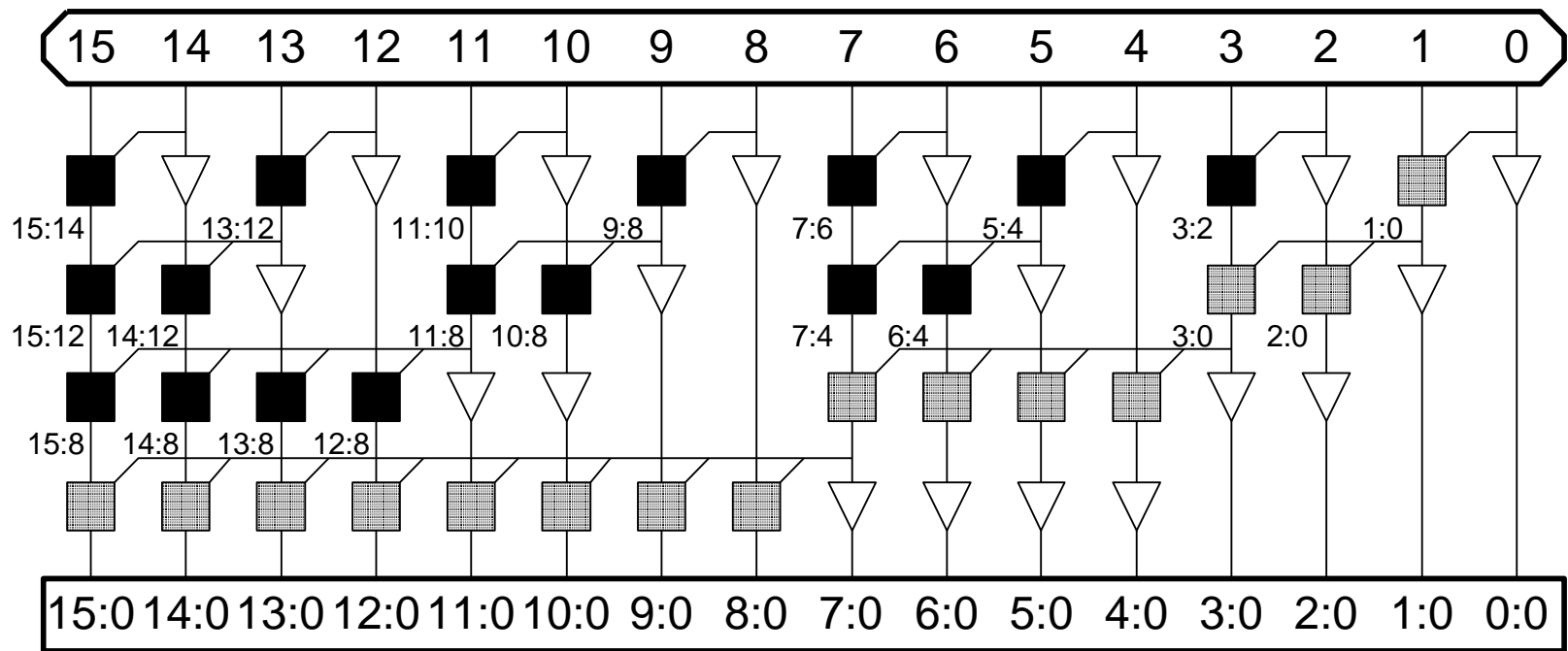

# Brent-Kung

 

# Kogge-Stone

 


# Tree Adder Taxonomy (David Harris)

---

- Ideal N-bit tree adder would have
  - $L = \log N$  logic levels
  - Fanout never exceeding 2
  - No more than one wiring track between levels
- Describe adder with 3-D taxonomy ( $l, f, t$ )
  - Logic levels:  $L + l$
  - Fanout:  $2^f + 1$
  - Wiring tracks:  $2^t$
- Known tree adders sit on plane defined by

$$l + f + t = L - 1$$

# Tree Adder Taxonomy

 

# Multiplication, Grade-School Level

---

- Product = Multiplicand \* Multiplier
  - Multiplicand scaled by each digit in the multiplier → partial products
  - These partial products are shifted and added up
- Base-10 example:  $119 * 182$ 
  - Partial products are:  $182 * 9 = 1638$ ,  $182 * 1 = 182$ ; and  $182 * 1 = 182$
  - Shift them and add them up

$$\begin{array}{r} 01638 \quad (9 * 182) \\ 01820 \quad (1 * 182) \\ \underline{18200} \quad (1 * 182) \\ 21658 \end{array}$$

- This is perhaps easier to read in binary...

# Multiplication, Grad-School Level

- Same basic idea, only now all digits are 0 or 1
  - But still have multiplicand, multiplier, and partial products
  - Ex:  $119 = 0111\ 0111$ ;  $182 = 1011\ 0110$


$$\begin{array}{r}
 . . . . . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0 \\
 . . . . . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ . \\
 . . . . . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ .\ . \\
 . . . . 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ .\ .\ . \\
 . . . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ .\ .\ .\ . \\
 . . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ .\ .\ .\ .\ . \\
 . 1\ 0\ 1\ 1\ 0\ 1\ 1\ 0\ .\ .\ .\ .\ .\ . \\
 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ .\ .\ .\ .\ .\ . \\
 \hline
 0\ 1\ 0\ 1\ 0\ 1\ 0\ 0\ 1\ 0\ 0\ 1\ 1\ 0\ 1\ 0 = 21658_{10}
 \end{array}$$

- Hm. Is there an easier notation for this operation?


 
# Dot Notation

- Rows of dots are partial products, either a “1” or a “0”
  - Number of dots corresponds roughly to total hardware needed
  - Height of dot structure corresponds roughly to total latency



- Result of multiplying two  $n$ -bit numbers is a  $2n$ -bit number
  - Integer operations keep the LSB  $n$  bits
  - Floating point operations keep the MSB  $n$  bits
    - Why?

# Adding up the PPs

---

- Main work of multiplier is to add all the partial products together
  - This is going to take a large number of adders (or)
  - A large number of cycles for one adder
- What things can we do to make this faster
  - Reduce the number of partial products
    - Called modified booth recoding
    - Look at two bits of multiplier and create one partial product
  - Make the adders very simple (but still fast)
    - Use just full adders, but use a carry-save number representation
  - Use trees to make the critical path shorter

# Technique #1: Coding to Reduce Work

---

- Observations:
  - Latency is determined by how many partial products I have
  - So reduce latency by reducing the number of partial products
  - If the multiplier bit is 0, there is no need to create a partial product
- Actually, we can do better
  - Suppose our multiplier is 0111 1111 (seven partial products)
  - Rewrite this as  $0111\ 1111 = 1000\ 0000 - 0000\ 0001$
  - Now I only need two partial products (but one is negative)
- This is called Booth encoding (1951)
  - Find strings of “1”s in the multiplier
  - Rewrite this as the difference between two numbers

# Basic Booth Recoding


- Apply this to our example:  $118 = 01110111$ 
  - Write 0111 as  $1000 - 0001$ ; this string shows up twice

$$\begin{array}{r}
 - \quad . \quad . \quad . \quad . \quad . \quad . \quad . \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \\
 + \quad . \quad . \quad . \quad . \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad . \quad . \quad . \\
 - \quad . \quad . \quad . \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad . \quad . \quad . \quad . \\
 + \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 0 \quad . \quad . \quad . \quad . \quad . \quad . \quad . \\
 \hline
 0 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 = 21658_{10}
 \end{array}$$

- This is an improvement; six partial products to four
- Not always helpful; imagine input of  $170 = 10101010$ 
  - Recoding into differences of two numbers doesn't help at all
  - No string of 1's to exploit
- Problem: Variable #s of PPs are hard to support in hardware
 
# Modified Booth Recoding

- Look at the multiplier three bits at a time
  - Try to figure out if we're starting, inside, or finishing a string of 1s
  - Overlap the three bits to help us figure this out
  - Really encoding just two bits at a time, but in context of three bits
- 16b multiplier always generates 9 partial products (PP0-PP8)
  - In general will create  $\text{floor}(0.5 \cdot (n+2))$  partial products
  - Pad the LSB with a 0, and the MSBs with enough 0s



# Modified Booth Recoding Rules

- Get different PPs depending on the rules (here, M=multiplicand)
  - If we're starting a string of 1's, put a  $-M$  at string's LSB
  - If we're ending a string of 1's, put a  $+M$  one left of string's MSB
  - If we're inside or outside a string, do nothing
  - Isolated 1's are treated as is

| Bit1 | Bit0 | Prev | Output | Comment  |
|------|------|------|--------|--|
| 0    | 0    | 0    | 0      | Outside a string of 1's. Do nothing            |
| 0    | 0    | 1    | $+M$   | Ended a string of 1's. Put $+M$ at MSB+1       |
| 0    | 1    | 0    | $+M$   | Isolated 1; treat as is                        |
| 0    | 1    | 1    | $+2M$  | Ended a string of 1's. Put $+M$ at MSB+1       |
| 1    | 0    | 0    | $-2M$  | Starting a string of 1's. Put $-M$ at LSB      |
| 1    | 0    | 1    | $-M$   | Start & end. Put $+M$ at MSB+1 and $-M$ at LSB |
| 1    | 1    | 0    | $-M$   | Starting a string of 1's. Put $-M$ at LSB      |
| 1    | 1    | 1    | 0      | Inside a string of 1's. Do nothing             |


- This needs  $+M$ ,  $-M$ ,  $+2M$ , and  $-2M$ 
  - $\pm 2M$  are easy: just take  $\pm M$  and shift it over a bit

# Carry-Save Adders

- If propagating the carry is slow, don't propagate the carry
  - “Doctor, it hurts when I do this.” “Then don't do this.”
- Carry-Save Adders represent the sum in a “redundant form”
  - $\text{Sum} = \text{sum\_1} + \text{sum\_2}$
  - Compute sum and carry, but don't propagate the carry
  - In other words,  $\text{Sum} = \text{sum\_without\_carries} + \text{carries}$
  - Need to do a final add with a carry propagate at the very end

```

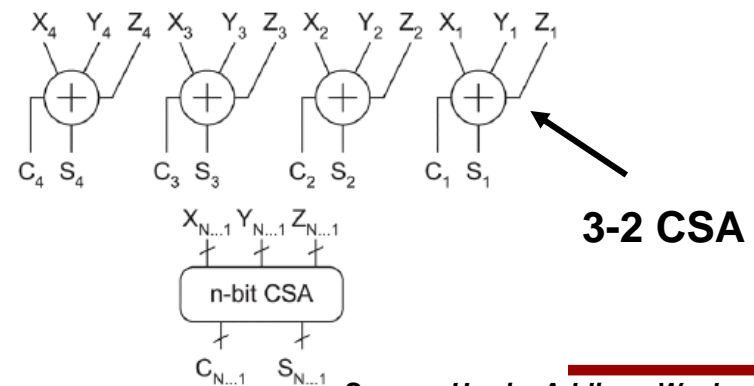
      0 1 0 1 0 1 1 0 1
    + 1 1 1 0 1 0 1 1 1
    =====
S   1 0 1 1 1 1 0 1 0
(Keep both S and C; add them later)
C  0 1 0 0 0 0 1 0 1
    
```



Source: Harris, Addison-Wesley, 2004
 
# Using CSAs In Multipliers


- Group terms into a tree of 3-2 CSAs
  - Sums stay in this column; carryouts go into left column (red)
  - Right column is giving me its carryouts (blue)





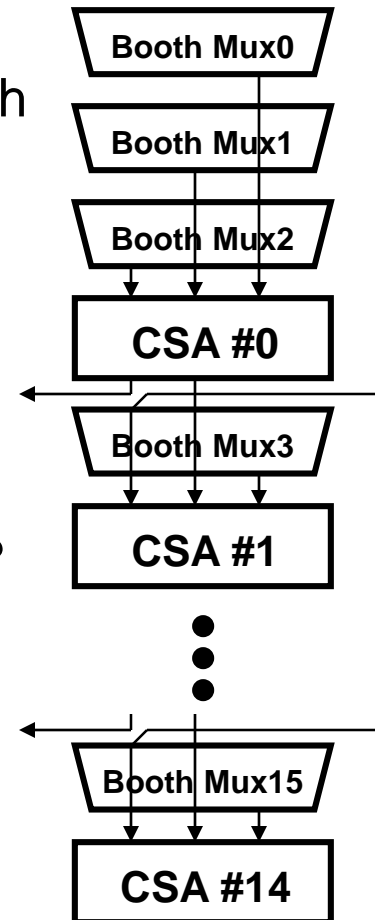
# Block Diagram of This Array

- This sample adder has 16 partial products
  - Therefore 13 CSAs, all in the critical path
  - First CSA takes 3 partial products
- Very regular datapath, fairly short wires
- Long latency due to extended critical path
  - What if we move away from linear path?
  - What about logarithmic structures?


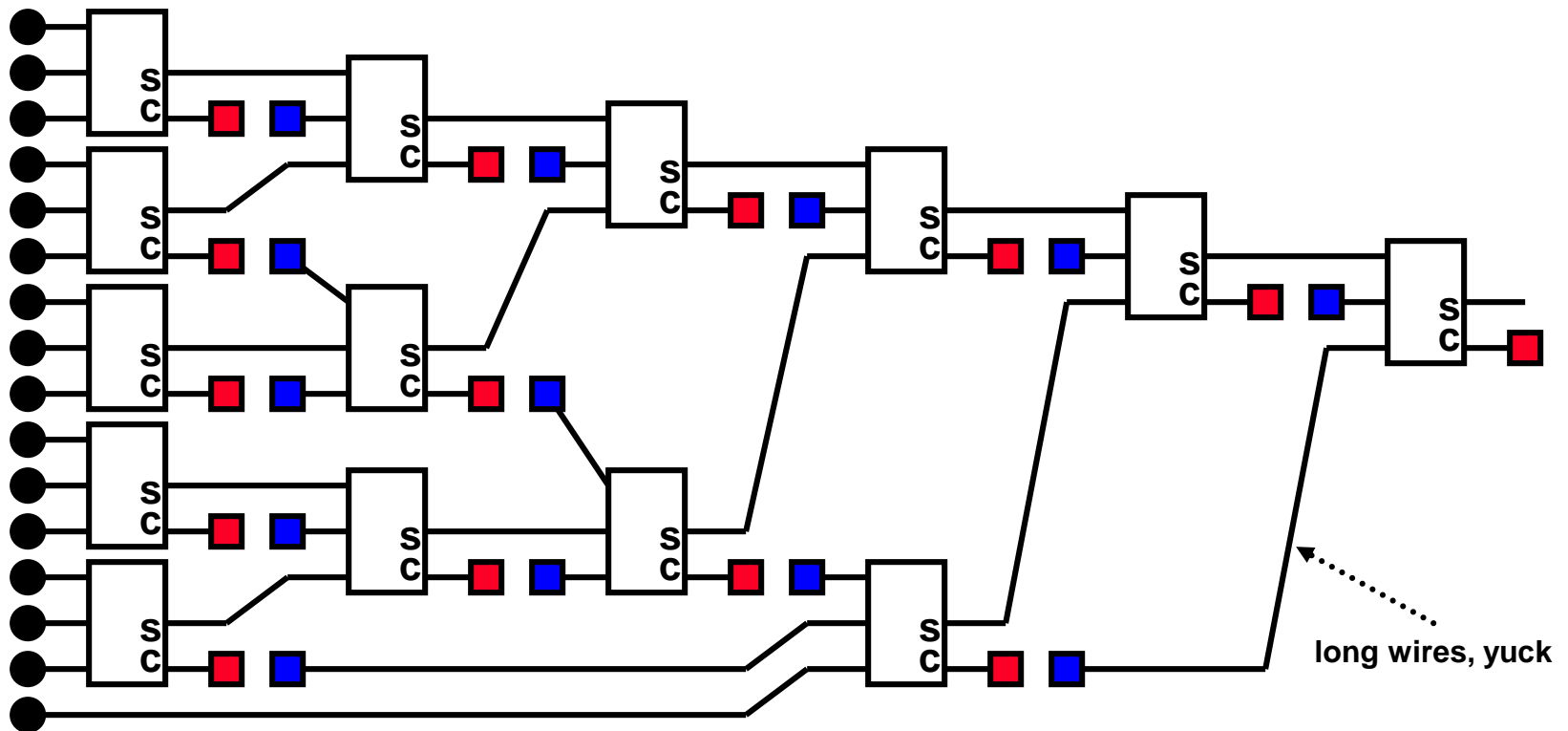
# Can Use Tree Here Too

- Group terms into a tree of 3-2 CSAs (a “Wallace Tree,” 1964)
  - Much shorter latency chain




# Problem With 3-2 Wallace Trees

---

- This seems good; critical path drops from 13 CSAs to 6
- But layout of this is messy
  - Irregular
  - Long wires that span multiple rows
  - 3-2 structures do not lend themselves nicely to trees
- Would much prefer to have a binary element for trees
 
## 4-2 Compressors

- Create a new element from two back-to-back 3-2 CSAs
  - Call this a 4-2 compressor: it “compresses” 4 inputs into 2 outputs




Source: Harris, Addison-Wesley, 2004

- “Wait,” you say. “This is really a 5-3 compressor.”
  - Yes, that’s right. Stop interrupting.
- This element allows for much more regular layout and wiring
 
# Using 4-2 Compressors In Multipliers

- Go back to the 16bit column example
  - In-between Cin and Cout terms (that make it 5-3) are not shown





# Logic Implementation of Full Adder

---

- $\text{Carry} = AB + AC + BC$ 
  - “At least two inputs are high”
  - Can be rewritten as  $AB + C(A+B)$
- $\text{Sum} = A \oplus B \oplus C = A \sim B \sim C + \sim A B \sim C + \sim A \sim B C + A B C$ 
  - “One or three inputs are high”
  
## + Transistor Level Implementation

- 32 Transistors (including inverters for A,B, and C)
- Various forms of 3-input XOR are possible



## + Shared Terms between Carry and Sum


---

- XOR's are somewhat expensive to implement
  - Actually very similar to multiplexers
    - Transmission gate logic only works for adders
- We can avoid them by taking another look at the problem
  - SUM=1 when 1 or 3 inputs are high (but not 0 or 2)
  - Carry =1 when 2 or 3 inputs are high
- Possible to reuse the carry term in sum to save some transistors
  - $\text{Sum} = ABC + \sim\text{Carry}(A+B+C)$
- Need to produce  $\sim\text{Carry}$  instead of Carry for this to work



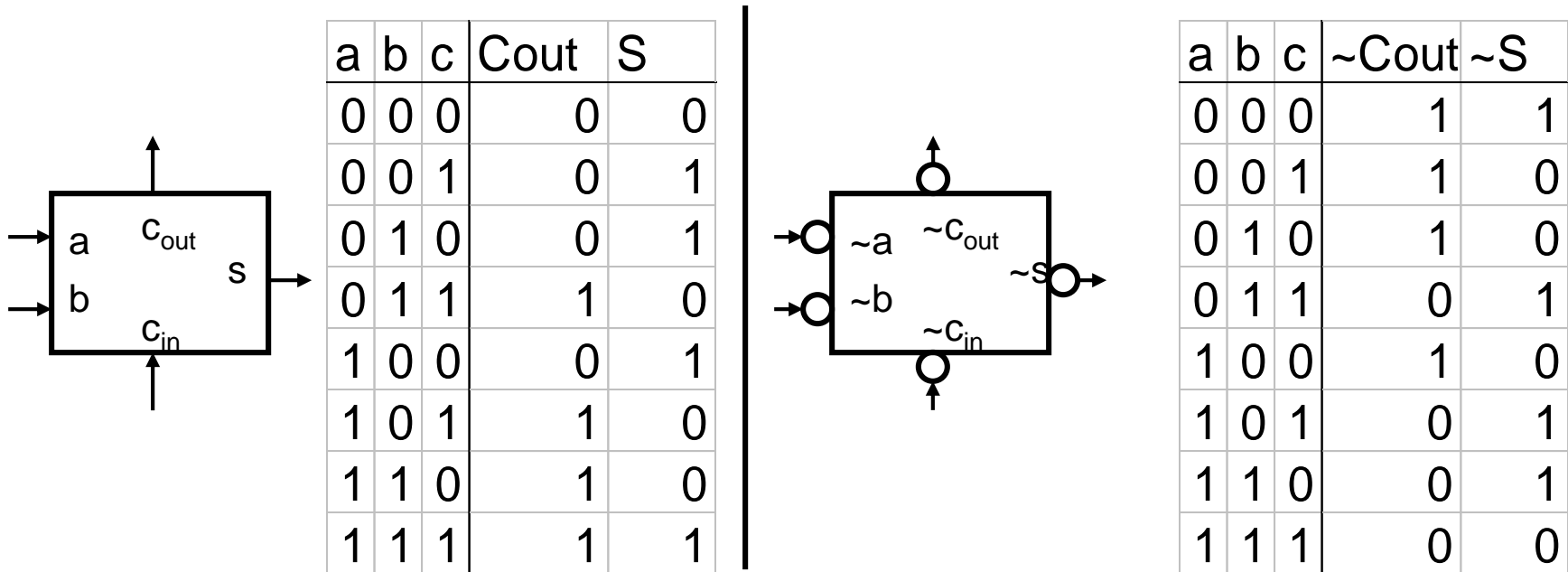
## + Aside: Interesting Property of Full Adders

- Inverting all the inputs creates an inverted output
  - Not true of normal gates (NANDs become NORs, etc)
- We can take advantage of this to produce  $\sim$ Carry



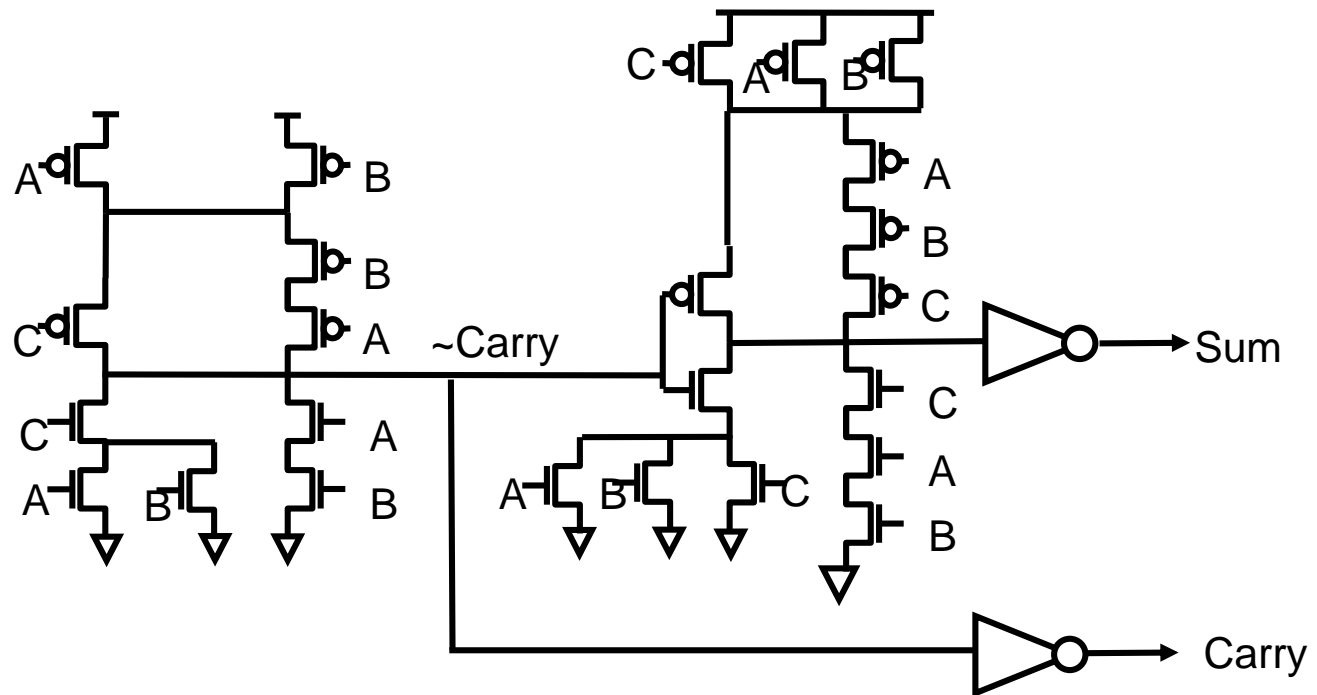
## + Full Adder With Reused Carry Term

- 28 Transistors (including inverters for Carry and Sum)
- Carry portion is identical to previous version
  - We inverted the inputs to get  $\sim\text{Carry}$



 
## + Subtle Improvement of Previous Carry Circuit

- We can make one more PMOS transformation
  - PMOS and NMOS are no longer duals, but it still works correctly
- Two advantages:
  - Three series PMOS transistors become two
  - Reduced capacitance on source of pMOS connected to C



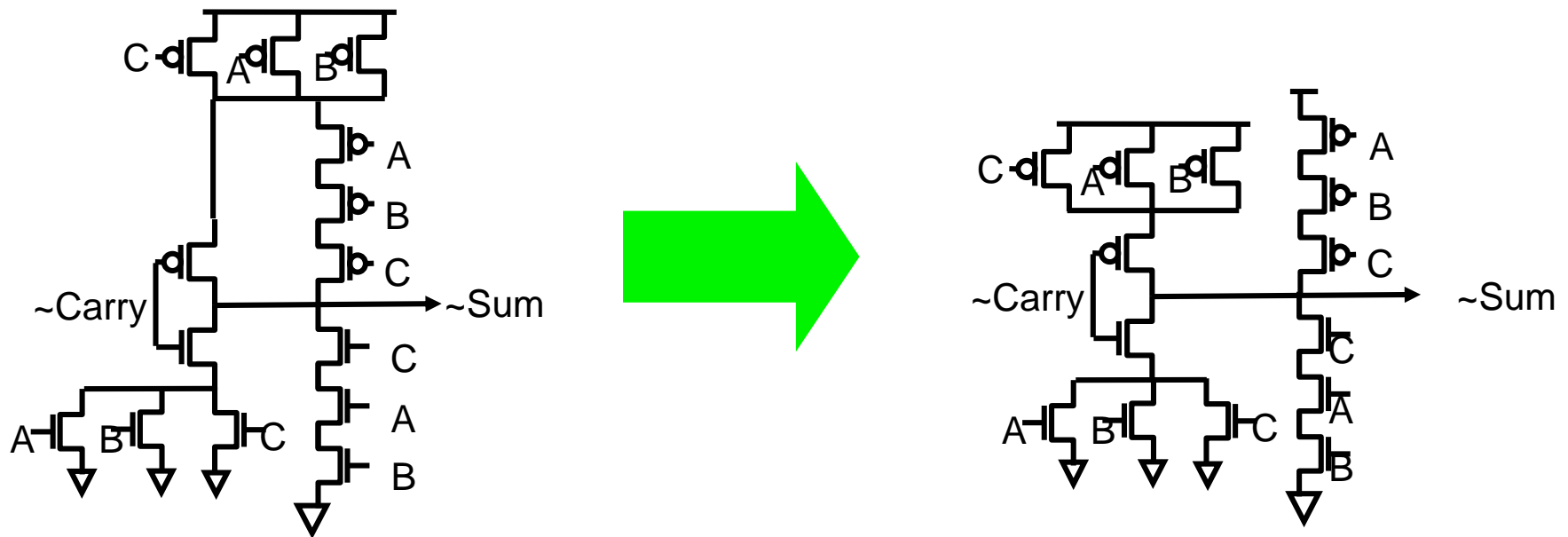
## + Improvement of Previous Sum Circuit

- Same type transformation as with Carry
- Similar advantages



 
# Critical Path of Ripple Carry Adders

- The final MSB can depend on the first carry
  - Consider the case of adding 0000001 to 01111111



 
# Critical Path of Ripple Carry Adders

- Our critical path has two gates per stage
  - One complex gate plus an inverter
- Can we reduce this to one?
  - If we can, do we want to?



 
# We Can: Inverting the Inputs

- What happens if we invert the inputs to the previous cell?
  - The outputs go from inverting to non-inverting
  - The same basic full adder cell can either take an inverted carry and produce a non-inverted one, or vice-versa




| a | b | c | $\sim C_{out}$ | $\sim S$ |
|---|---|---|----------------|----------|
| 0 | 0 | 0 | 1              | 1        |
| 0 | 0 | 1 | 1              | 0        |
| 0 | 1 | 0 | 1              | 0        |
| 0 | 1 | 1 | 0              | 1        |
| 1 | 0 | 0 | 1              | 0        |
| 1 | 0 | 1 | 0              | 1        |
| 1 | 1 | 0 | 0              | 1        |
| 1 | 1 | 1 | 0              | 0        |

 

| $\sim a$ | $\sim b$ | $\sim c$ | $C_{out}$ | $S$ |
|----------|----------|----------|-----------|-----|
| 0        | 0        | 0        | 0         | 0   |
| 0        | 0        | 1        | 0         | 1   |
| 0        | 1        | 0        | 0         | 1   |
| 0        | 1        | 1        | 1         | 0   |
| 1        | 0        | 0        | 0         | 1   |
| 1        | 0        | 1        | 1         | 0   |
| 1        | 1        | 0        | 1         | 0   |
| 1        | 1        | 1        | 1         | 1   |
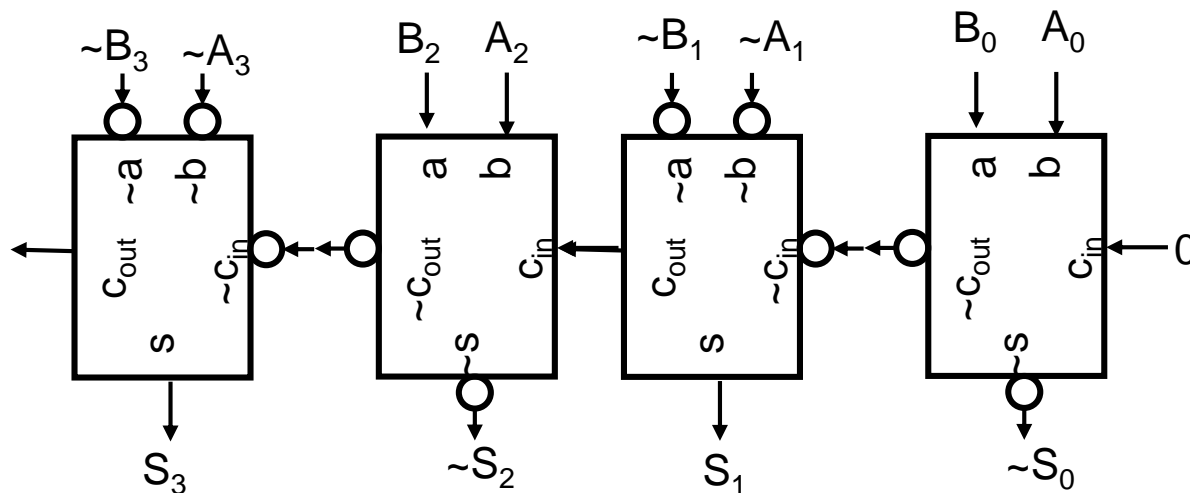
# Alternating True and Complement Carries


- Concatenating Full Adders without inverters works fine
  - Inversions on carry chains cancel one another out
  - Need to invert sum output on even numbered stages
  - Need to invert A and B inputs on odd numbered stages
    - Not in critical path





 
# Evaluating Inverting Versus Non Inverting

- Fewer Stages is not necessarily better
  - Need to look at the total path effort
  - Find the “appropriate” number of stages
- Each Cout drives two gates
  - Next stage, and the sum gate (all the red circles)
- What is the stage effort?
  - Depends on the relative sizing of the devices



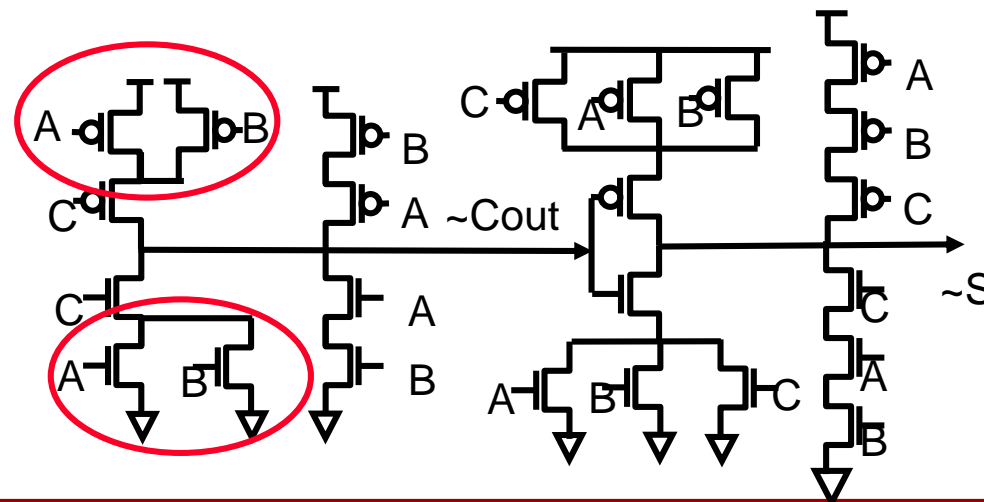
# Speeding up the Inverting Full Adder

- Key is to reduce logical effort and branching effort
  - Slow down A and B paths to speed up Carry path
- Reducing logical effort
  - Make circled devices wide to reduce their resistance
    - Reduces logic effort for the C input
    - In the limit, LE will come close to 1 (inv)


 
# Speeding up the Inverting Full Adder

- Reducing branching effort
  - Make circled devices small to reduce their loading
    - Since min width is usually specified, need to make the main drive large compared to the side loads



# Layout

- Clever layout circumvents usual line of diffusion
  - Use wide transistors on critical path
  - Eliminate output inverters

