

EE 431: COMPUTER-AIDED DESIGN OF VLSI DEVICES

MOSFET Parasitics & Delay Estimation



Nishith N. Chakraborty

October, 2024

MOSFET CAPACITANCE

- Any two conductors separated by an insulator have capacitance
- Gate to channel capacitor is very important
 - Creates channel charge necessary for operation
- Source and drain have capacitance to body
 - Across reverse-biased diodes
 - Called diffusion capacitance because it is associated with source/drain diffusion


CAPACITANCE COMPONENTS

  




$$C_{gate} = \frac{\epsilon_{ox}}{t_{ox}} WL$$

GATE CAPACITANCE

 
- Approximate channel as connected to source
- $C_g = \epsilon_{ox} WL/t_{ox} = C_{ox} WL = C_{permicron} W$
- $C_{permicron}$ is typically about 2 fF/ μm



GATE CAPACITANCE

   


| Capacitance | Cutoff | Linear | Saturation |
|-----------------|---------------------|--|--|
| $C_{gb(total)}$ | $C_{ox}WL_{actual}$ | 0 | 0 |
| $C_{gs(total)}$ | C_{GSO} | $\frac{1}{2}C_{ox}WL_{actual} + C_{GSO}$ | $\frac{2}{3}C_{ox}WL_{actual} + C_{GSO}$ |
| $C_{gd(total)}$ | C_{GDO} | $\frac{1}{2}C_{ox}WL_{actual} + C_{GDO}$ | C_{GDO} |

 


$$L_{actual} = L - 2L_D$$

Most important regions
in digital design:
Saturation and Cut-off

GATE CAPACITANCE

 

 (a) C_{GC} as a function of V_{GS} (with $V_{DS}=0$)




(b) C_{GC} as a function of the degree of saturation


| Operation Region | C_{GCB} | C_{GCS} | C_{GCD} | C_{GC} | C_G |
|------------------|-----------------|-----------------|----------------|-----------------|-------------------------|
| Cutoff | $\leq C_{ox}WL$ | 0 | 0 | $\leq C_{ox}WL$ | $\leq C_{ox}WL + 2C_oW$ |
| Resistive | 0 | $C_{ox}WL / 2$ | $C_{ox}WL / 2$ | $C_{ox}WL$ | $C_{ox}WL + 2C_oW$ |
| Saturation | 0 | $(2/3)C_{ox}WL$ | 0 | $(2/3)C_{ox}WL$ | $(2/3)C_{ox}WL + 2C_oW$ |

DIFFUSION CAPACITANCE

 - C_{sb} , C_{db}
- Undesirable, called parasitic capacitance
- Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diffusion
 - $\frac{1}{2} C_g$ for uncontacted
 - Varies with process




DIFFUSION CAPACITANCE

 





$$C_{diff} = C_{bottom} + C_{sw} = C_j \times AREA + C_{jsw} \times PERIMETER$$

$$= C_j L_S W + C_{jsw} (2L_S + W)$$

 


Higher capacitance in FinFETs compared to bulk MOSFETs (due to 3D structure)

RC EQUIVALENT DELAY MODEL

 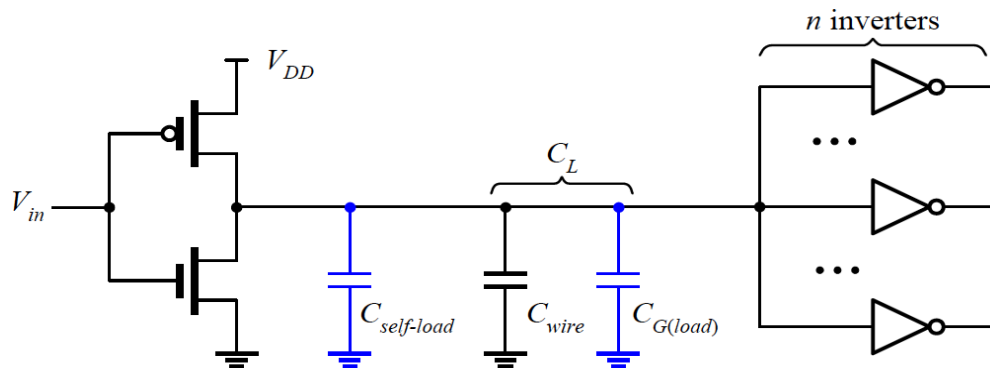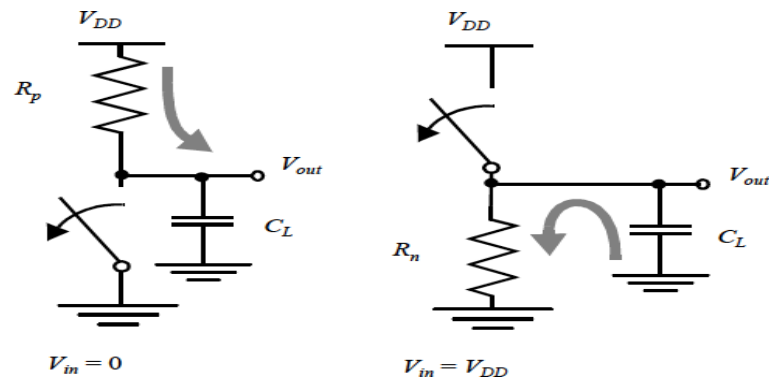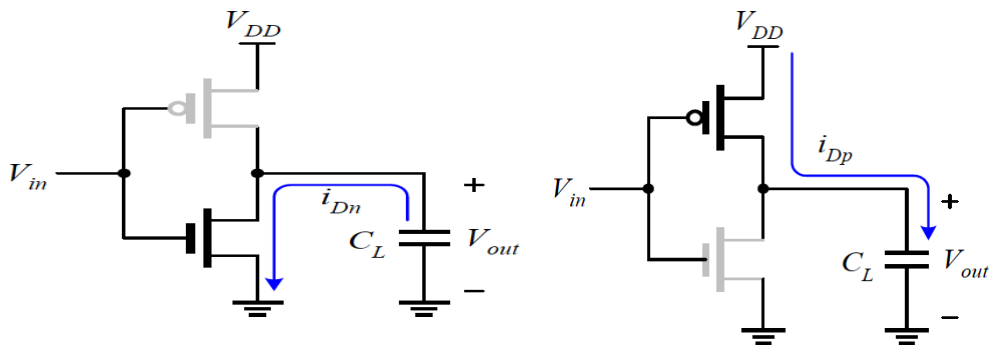

FAN-OUT, FAN-IN AND DELAY

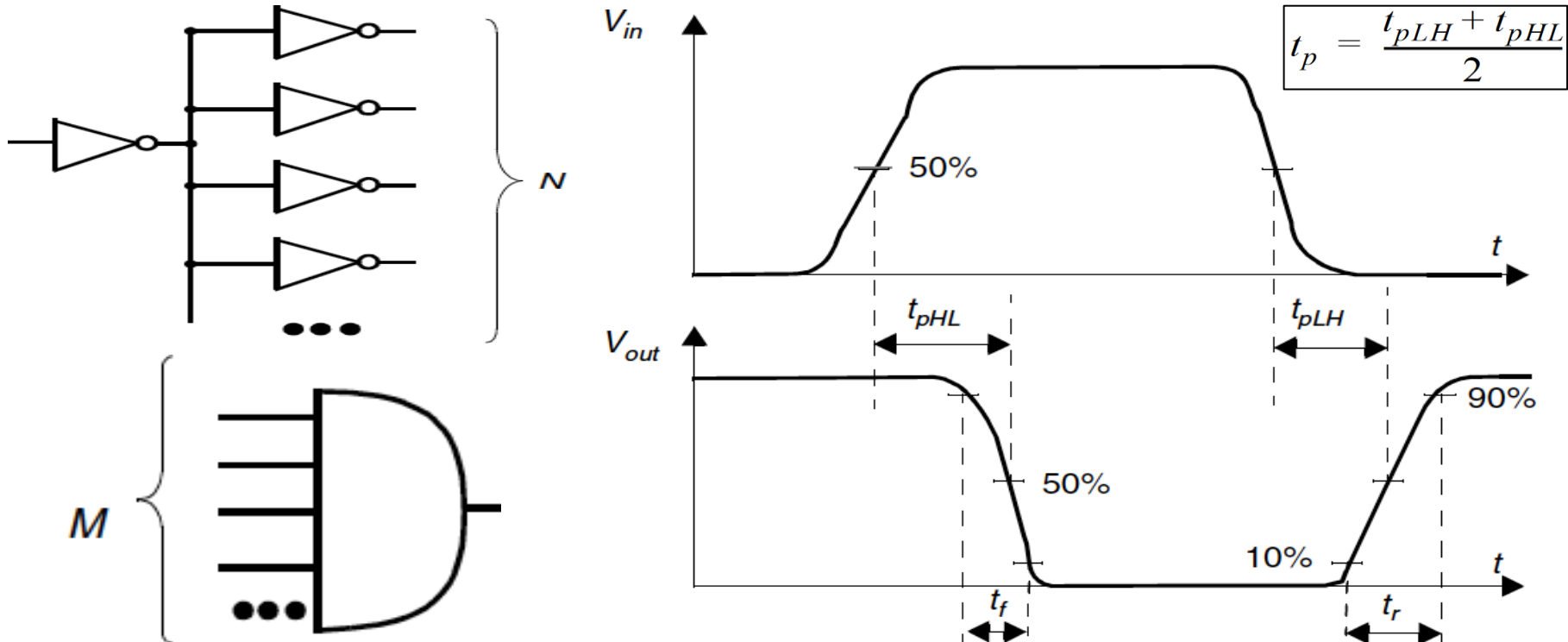


DELAY DEFINITIONS

- t_{pdr} : rising propagation delay
 - From input to rising output crossing $V_{\text{DD}}/2$
- t_{pdf} : falling propagation delay
 - From input to falling output crossing $V_{\text{DD}}/2$
- t_{pd} : average propagation delay
 - $t_{\text{pd}} = (t_{\text{pdr}} + t_{\text{pdf}})/2$
- t_{r} : rise time
 - From output crossing $0.1 V_{\text{DD}}$ to $0.9 V_{\text{DD}}$
- t_{f} : fall time
 - From output crossing $0.9 V_{\text{DD}}$ to $0.1 V_{\text{DD}}$

SIMULATED INVERTER DELAY

 - Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too! But simulations take time to write



DELAY ESTIMATION

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- The step response usually looks like a 1st order RC response with a decaying exponential.
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use effective resistance R
 - So that $t_{pd} = RC \ln 2$, lets just replace $R \ln 2$ with R , so $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC DELAY MODEL

- Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit sized NMOS has resistance R , capacitance C
 - Unit sized PMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width




RC VALUES

- Capacitance
 - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width
 - Values similar across many processes
- Resistance
 - $R \sim 6 \text{ K}\Omega \cdot \mu\text{m}$ in 0.6um process
 - Improves with shorter channel lengths
- Unit transistors
 - May refer to minimum contacted device
 - Or maybe 1 μm wide device
 - Doesn't matter as long as you are consistent


INVERTER DELAY ESTIMATION

 - Estimate the delay of a “fanout-of-1” inverter




INVERTER DELAY ESTIMATION

 - Estimate the delay of a “fanout-of-1” inverter



INVERTER DELAY ESTIMATION

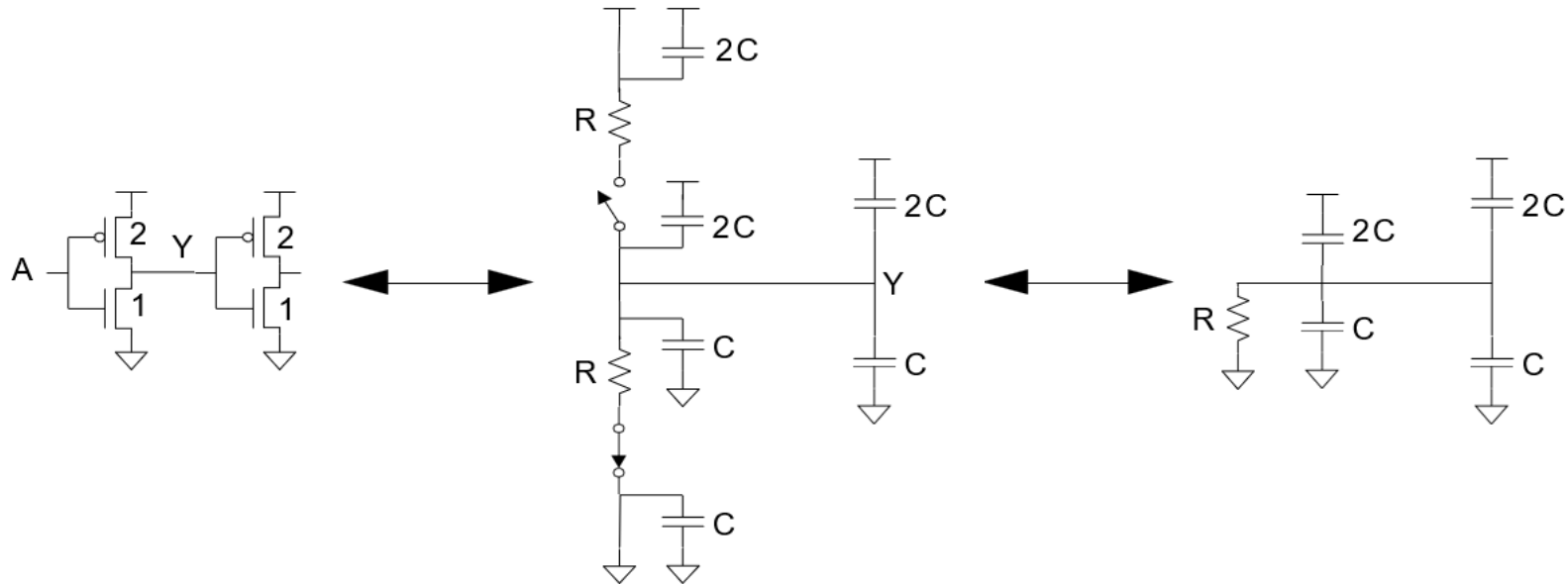
- Estimate the delay of a “fanout-of-1” inverter



$$d = 6RC$$

 
EXAMPLE: 3-INPUT NAND GATE

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



 
EXAMPLE: 3-INPUT NAND GATE

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).




 
EXAMPLE: 3-INPUT NAND GATE

- Annotate the 3-input NAND gate with gate and diffusion capacitance.




  EXAMPLE: 3-INPUT NAND GATE

- Annotate the 3-input NAND gate with gate and diffusion capacitance. Show the rise and fall paths.



EXAMPLE: $Y = A(B + C) + DE$

 

PMOS sizing: For a unit PMOS transistor, the effective resistance with the width k is given by $2R/k$.

By looking at the pull-up network in the above circuit, we should find out the worst-case or the longest path to VDD. In the above network, the path E-C-B is the longest path. So we can write the equation $(2R/k) + (2R/k) + (2R/k) = R$, where R is the effective resistance. The equation gives the value of $k = 6$. Therefore the k value transistors E, C, and B will be 6.

One more path D-C-B also contributes to the worst-case or longest path, So the k value of the transistor D also becomes 6. The transistor A is equivalent to two transistors B and C (by looking at the circuit). Therefore we can write $2R/k = 2 * 2R/6$ Since we know the k values of B and C transistors. So k for A is 3.

NMOS sizing:

For a unit NMOS transistor, the effective resistance with the width k is given by R/k .


In the above network, the worst-case or the longest path can be seen is with two transistors. (The paths A-B, A-C, and D-E). So we can write the relation $2 * R/k = R$, So the value of k of all the NMOS transistors will be 2 since all are in the longest path.

ELMORE DELAY

- ON transistors look like resistors
- Pullup or pulldown network modeled as RC ladder
- Elmore delay of RC ladder



$$t_{pd} \approx \sum_{\text{nodes } i} R_{i-\text{to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



 
 
EXAMPLE: 2-INPUT NAND GATE

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.




 
 
EXAMPLE: 2-INPUT NAND GATE

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.



 
 
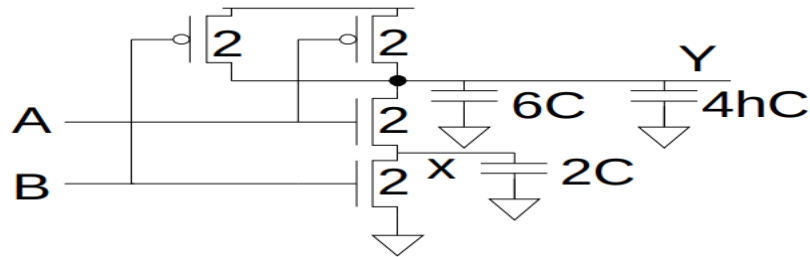
EXAMPLE: 2-INPUT NAND GATE

- Estimate worst-case **rising** and falling delay of 2-input NAND driving h identical gates.



  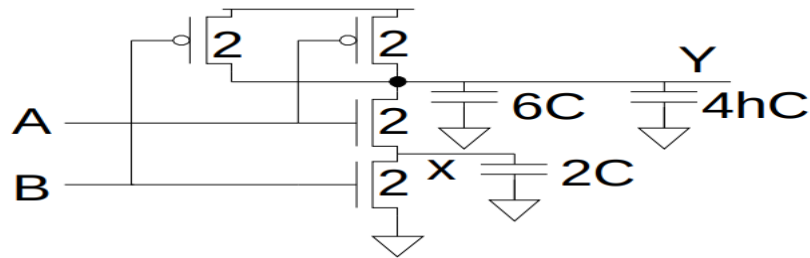EXAMPLE: 2-INPUT NAND GATE




- Estimate worst-case **rising** and falling delay of 2-input NAND driving h identical gates.



$$t_{pdr} = (6 + 4h) RC$$

 
 
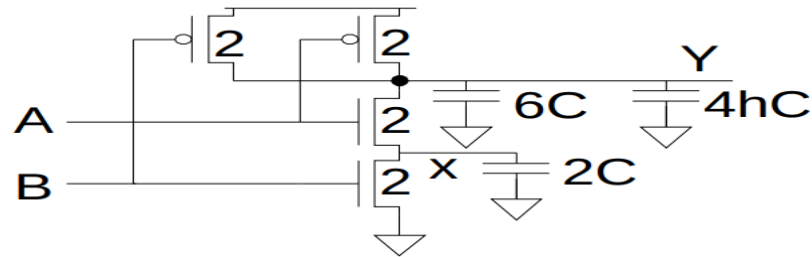
EXAMPLE: 2-INPUT NAND GATE

- Estimate worst-case rising and **falling** delay of 2-input NAND driving h identical gates.



   EXAMPLE: 2-INPUT NAND GATE

- Estimate worst-case rising and **falling** delay of 2-input NAND driving h identical gates.



$$t_{pdf} = (2C) \left(\frac{R}{2} \right) + \left[(6 + 4h) C \right] \left(\frac{R}{2} + \frac{R}{2} \right)$$


$$= (7 + 4h) RC$$

DELAY COMPONENTS

- Delay has two parts
 - Parasitic delay
 - 6 or 7 RC
 - Independent of load
 - Effort delay
 - 4h RC
 - Proportional to load capacitance


CONTAMINATION DELAY

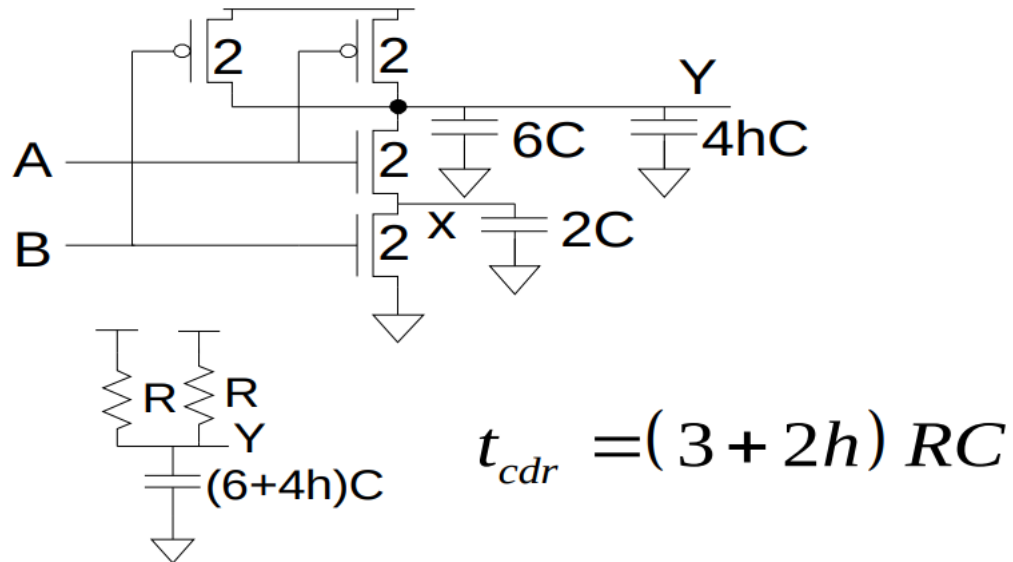- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If both inputs fall simultaneously



DIFFUSION CAPACITANCE

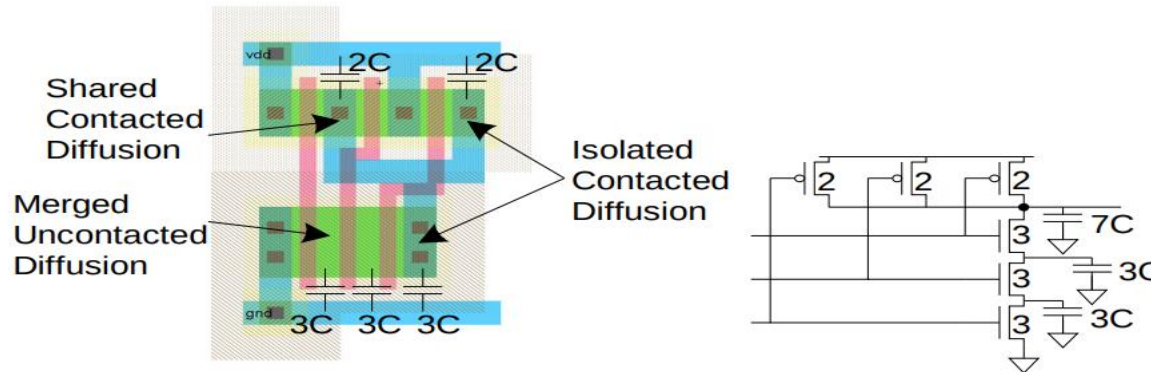- We assumed contacted diffusion on every s / d.
- Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



Thank you!