

EE 531: ADVANCED VLSI DESIGN


Logic Synthesis: Part 2

Nishith N. Chakraborty

January, 2025


CONSTRAINT DEFINITION

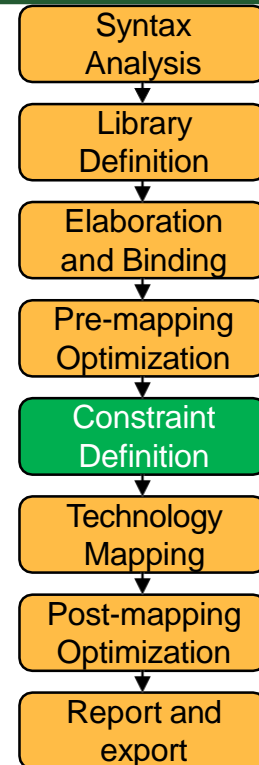- Following **Elaboration**, the design is loaded into the synthesis tool and stored inside a data structure.
- Hierarchical ports (inputs/outputs) and registers can be accessed by name.
- At this point, we can load the design constraints in SDC format.
- Carefully check that all constraints were accepted by the tool!



TECHNOLOGY MAPPING

- Technology mapping is the phase of logic synthesis when gates are selected from a technology library to implement the circuit.
- Why technology mapping?
 - Straight implementation may not be good.
 - For example, $F=abcdef$ as a 6-input AND gate causes a long delay.
 - Gates in the library are pre-designed, they are usually optimized in terms of area, delay, power, etc.
 - Fastest gates along the critical path, area-efficient gates (combination) off the critical path.
- Can apply a **minimum cost tree-covering** algorithm to solve this problem.

 

TECHNOLOGY MAPPING ALGORITHM

- Using a **recursive tree-covering algorithm**, we can easily, and almost optimally, **map a logic network** to a **technology library**.
- This process incurs three steps:
 - **Map netlist** and tech library to simple gates
 - Describe the netlist with only NAND2 and NOT gates
 - Describe SC library with NAND2 and NOT gates and associate a **cost** with each gate
 - **Tree-ifying** the input netlist
 - Tree covering can only be applied to trees!
 - Split tree at all places, where fanout ≥ 2
 - **Minimum Cost Tree** matching
 - For each node in your tree, recursively find the minimum cost target pattern at that node.
- Let us briefly go through these steps

STEP 1: SIMPLE GATE MAPPING

- Apply **De Morgan** laws to your Boolean function to make it a collection of NAND2 and NOT gates.
- Let's take the example of multi-level logic minimization:

$$\begin{aligned} t_1 &= d + e; \\ t_2 &= b + h; \\ t_3 &= at_2 + c; \\ t_4 &= t_1t_3 + fgh; \\ F &= t_4'; \end{aligned}$$

$$t_1 = d + e = \text{NAND}(\bar{d}, \bar{e})$$


$$t_2 = b + h = \text{NAND}(\bar{b}, \bar{h})$$

$$t_3 = at_2 + c = \overline{\overline{at_2} \cdot \bar{c}} = \text{NAND}(\text{NAND}(a, t_2), \bar{c})$$

$$t_4 = t_1t_3 + fgh = \text{NAND}(\overline{t_1t_3}, \overline{fgh})$$

$$fgh = \overline{\overline{fh} \cdot \bar{g}} = \overline{\overline{fh} \cdot g} = \text{NAND}(\overline{\text{NAND}(f, h)}, g)$$

$$F = \bar{t_4}$$

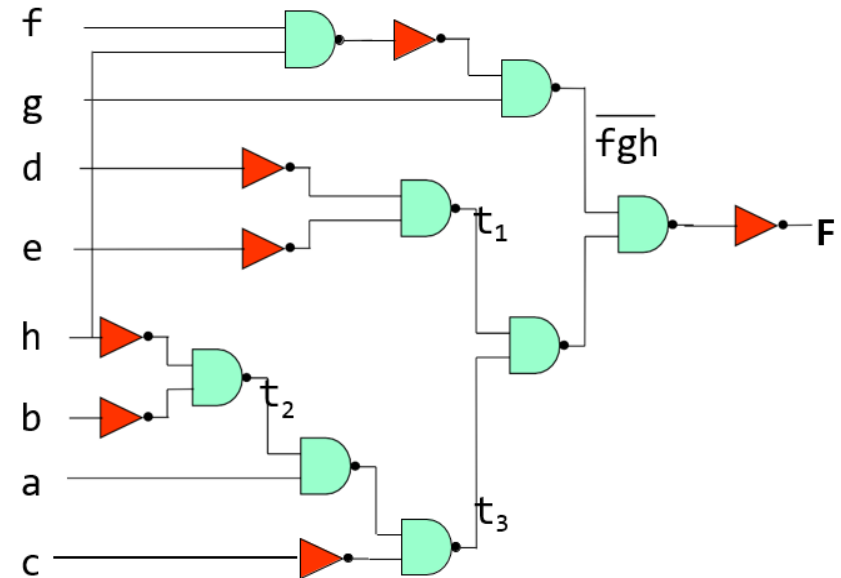


STEP 1: SIMPLE GATE MAPPING

- And then, given a set of gates (standard cell library) with cost metrics (area/delay/power):




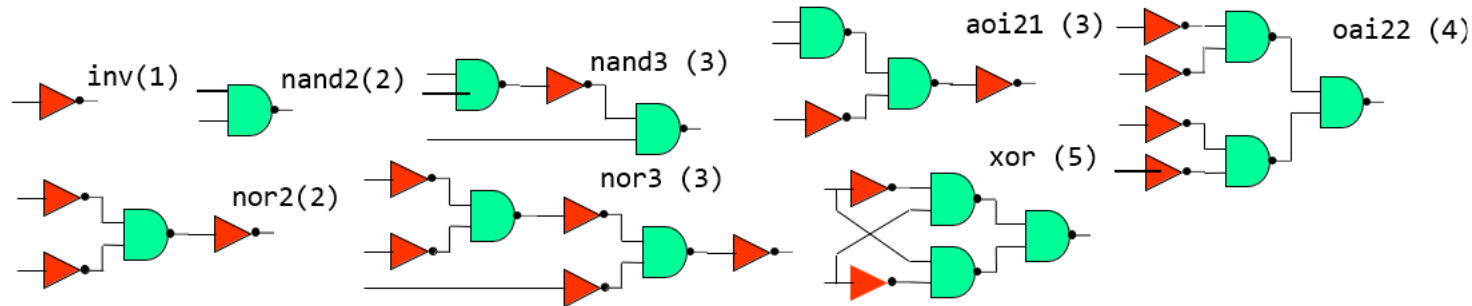- We need to define the gates with the same NAND2/NOT set:



STEP 2: TREE-IFYING

 - To apply a tree covering algorithm, we must work on a tree!
 - Is any given logic network a tree?
 - No!
 - We must break the tree at any node with fanout ≥ 2




STEP 3: MINIMUM TREE COVERING

- Now, we can apply a recursive algorithm to achieve a minimum cover:

- Start at the output of the graph.
- For each node, find all the matching target patterns.
- The cost of node i for using gate g is:

$$\text{cost}(i) = \min_k \left\{ \text{cost}(g_i) + \sum \text{cost}(k_i) \right\}$$

- where k_i are the inputs to gate g .

 

STEP 3: MINIMUM TREE COVERING


- Now, we can apply a recursive algorithm to achieve a minimum cover:

- Start at the output of the graph.
- For each node, find all the matching target patterns.
- The cost of node i for using gate g is:


$$\text{cost}(i) = \min_k \left\{ \text{cost}(g_i) + \sum \text{cost}(k_i) \right\}$$

- where k_i are the inputs to gate g .
- For simplicity, we will redraw our graph and show an example:


 
- Every NOT is just an empty circle: **I**
- Every NAND is just a full circle: **N**
- Every input is just a box: **A**




MINIMUM TREE COVERING: EXAMPLE

 



MINIMUM TREE COVERING: EXAMPLE

  

 f: NOT $2 + \min(w)$
AND2 $4 + \min(y) + \min(z)$
AOI21 $6 + \min(x)$



MINIMUM TREE COVERING: EXAMPLE

  

f: NOT $2 + \min(w)$

AND2 $4 + \min(y) + \min(z)$


AOI21 $6 + \min(x)$

w: NAND2 $3 + \min(y) + \min(z) = 3 + 2 + 6 = 11$



y: NOT 2

z: NAND2 $3 + \min(x) = 3 + 3 = 6$

x: NAND2 3

 

MINIMUM TREE COVERING: EXAMPLE

  

f: NOT $2 + \min(w) = 2 + 11 = 13$

AND2 $4 + \min(y) + \min(z) = 4 + 2 + 6 = 12$

AOI21 $6 + \min(x) = 6 + 3 = 9$


w: NAND2 $3 + \min(y) + \min(z) = 3 + 2 + 6 = 11$

y: NOT 2

z: NAND2 $3 + \min(x) = 3 + 3 = 6$

x: NAND2 3

NAND2

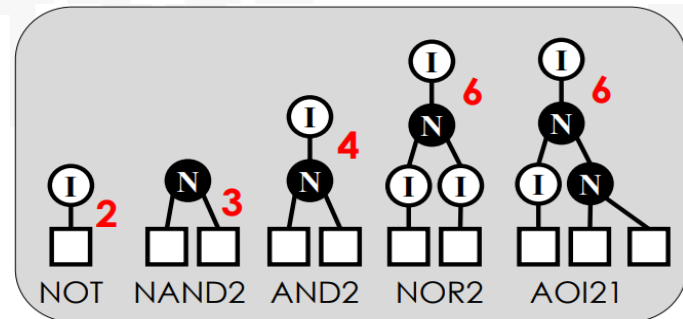


Verilog for Synthesis: Revisited

VERILOG TO CIRCUIT

- Let's take a simple 4→2 encoder as an example:
 - Take a one-hot encoded vector and output the position of the '1' bit.
 - One possibility would be to describe this logic with a nested if-else block:
 - The result is known as “priority logic”
 
```
always @(x)
begin : encode
  if (x == 4'b0001) y = 2'b00;
  else if (x == 4'b0010) y = 2'b01;
  else if (x == 4'b0100) y = 2'b10;
  else if (x == 4'b1000) y = 2'b11;
  else y = 2'bxx;
end
```






VERILOG TO CIRCUIT

- It would have been better to use a **case** construct:


- All cases are matched in **parallel**
- And better yet, synthesis can **optimize** away the constants and other Boolean equalities:
   
```
always @(x)
begin : encode
case (x)
4'b0001: y = 2'b00;
4'b0010: y = 2'b01;
4'b0100: y = 2'b10;
4'b1000: y = 2'b11;
default: y = 2'bxx;
endcase
end
```



A FEW POINTS ABOUT OPERATORS


- Logical operators map into primitive logic gates
- Arithmetic operators map into adders, subtractors, ...
 - Unsigned or signed 2's complement
 - Model carry: target is one-bit wider than source
 - Watch out for *, %, and /
- Relational operators generate comparators
- Shifts by constant amount are just wire connections
 - No logic involved
- Variable shift amounts a whole different story → shifter
- Conditional expression generates logic or MUX

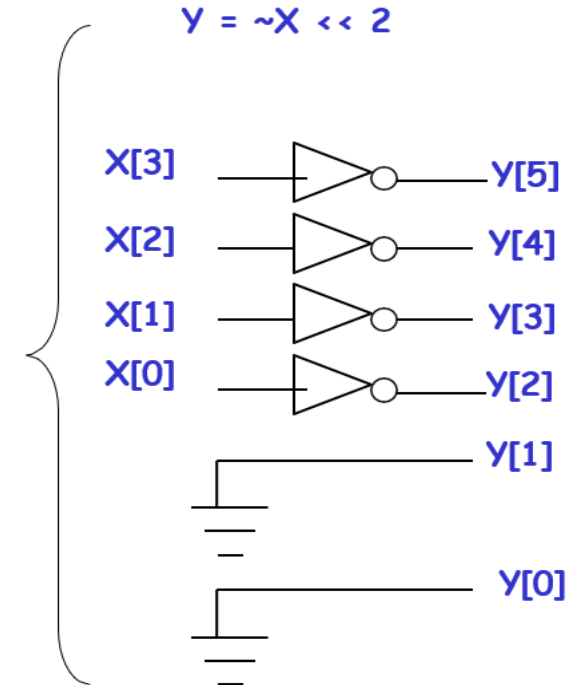


DATAPATH SYNTHESIS

- Complex operators (Adders, Multipliers, etc.) are implemented in a special way
 - E.g. Type of multiplier
 
```
module mult (d1, d2, do);
input [7:0] d1, d2;
output [15:0] do;
assign do = d1 * d2;
endmodule
```



OPTIMIZATION

 

OPTIMIZATION OPTIONS FOR SYNTHESIS


- Another look at RTL to physical layout (GDSII*) design flows
- Metrics used for optimization
 - Speed
 - Area
 - Power
 - Others?
- ASIC/SoC design choices that allow optimizations

TIMING DRIVEN SYNTHESIS

- Traditionally, timing has been one of the major drivers in ASIC/SoC design
- The goal is to minimize the delay on the *critical path* of the design so that the frequency is maximized
- CAD tools must include accurate and robust models for estimating the delay through the circuit(s)
- During synthesis, several choices can be made to reduce delay:
 - Optimize number of logic levels
 - Logic family used (if in standard cell library)
 - Cell sizing (usually have multiple sized std. cells)



HOW TO OPTIMIZE TIMING?

 - There are many 'transforms' that the synthesizer applies to the logic to improve the cost function:
 - Resize cells
 - Buffer or clone to reduce load on critical nets
 - Decompose large cells
 - Swap connections on commutative pins or among equivalent nets
 - Move critical signals forward
 - Pad early paths
 - Area recovery
- Simple example:
 - Double inverter removal transform:




RESIZING, CLONING AND BUFFERING

  
- Resize a logic gate to better drive a load:



 - Or make a copy (clone of the gate) to distribute the load:




- Or just buffer the fanout net:

 


REDESIGN FAN-IN/FAN-OUT TREES

- Redesign Fan-In Tree

 


- Redesign Fan-Out Tree

 

DECOMPOSITION AND SWAPPING

 - Consider decomposing complex gates into less complex ones:



- Swap commutative pins:

➤ Simple sorting on arrival times and delays can help



WORST NEGATIVE SLACK


- Design Vision (and many other tools) uses **Worst Negative Slack (WNS)** to achieve timing requirements
- Slack = Design Delay – Predicted Delay
 - Design Frequency is essentially the target which is usually higher than Market Frequency
 - Predicted Frequency is the frequency of the current design determined by low-level simulation
- Negative slack occurs when the design does not meet the timing requirements
- Worst Negative Slack refers to the critical path, the path with the most delay

RETIMING THE DESIGN

- **Retiming:** technique for improving performance of sequential circuits by repositioning registers
 - Reduces cycle time or area with no I/O latency change
- Pipelining is a subset of retiming
- Retiming redistributes sequential elements at appropriate locations to meet requirements
- Retiming does not change combinational logic


RETIMING FOR TIMING

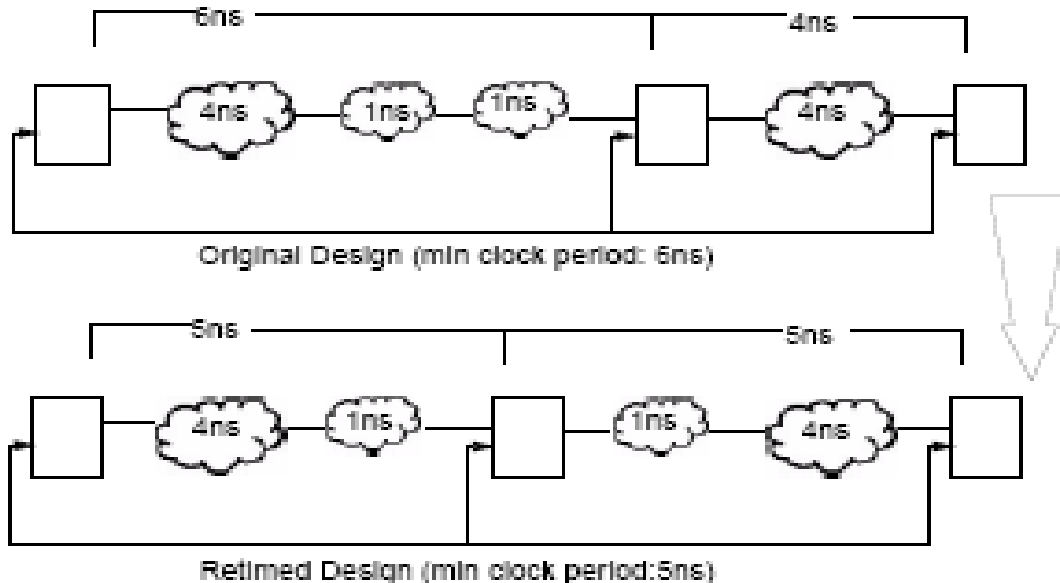- Improving clock period or timing slack common
- Design Compiler distributes the registers within the design to provide minimum cycle time



RETIMING FOR AREA

 - When retiming for area, Design Vision moves registers to minimize register count without worsening the critical path in the design



POWER AS A DESIGN METRIC

- Power determined by four major factors:
 - Capacitance being driven (C)
 - Voltage (V_{DD})
 - Frequency (f)
 - Activity factor (α)

$$P = \alpha \cdot C \cdot V_{DD}^2 \cdot f$$


- Low-power design techniques focus on these factors for controlling the power consumption of a design

LOW-POWER DESIGN TECHNIQUES


- Dynamic Voltage Scaling (DVS)
 - lower V_{DD} during runtime for quadratic savings
 - Frequency scaling
 - Sleep mode transistors
-
- Note: These are all techniques for reducing dynamic power; as technology scales, static power is becoming more of a concern

CLOCK GATING

 - Dynamic power control through synthesis typically due to clock gating
- Usually this means shutting off the clock to flip flop(s)
- Example to the right:
 - Conceptually the same
 - Implementation 1 clocks the flip flop every cycle
 - Implementation 2 only clocks when enabled
 - the lower power design



Implementation 1

 


Implementation 2


CLOCK GATING LEVELS

- Block level (Global) clock-gating
 - If certain operating modes do not use an entire module/component, a clock gate should be defined in the RTL.
- Register level (Local) clock-gating
 - However, even at the register level, if a flip-flop doesn't change its output, internal power is still dissipated due to the clock toggling.
 - This is very typical of an enabled signal sampling and therefore can be automatically detected and gated by the synthesis tool.

Global Clock Gating

 

Local Clock Gating

 

SYNTHESIZED CLOCK GATING

- To implement clock gating for power control during synthesis, tools analyze design at elaboration stage
- Most likely, gating structures are not applied to every register – cost in power of gating would exceed savings on the flip flops
- Synthesis tool tries to find gating enable signals within the design that can control the clock for a register bank

CLOCK GATING INSTANTIATION

- Local clock gating: 3 methods
 - Logic synthesizer finds and implements local gating opportunities
 - RTL code explicitly specifies clock gating
 - Clock gating cell explicitly instantiated in RTL
- Global clock gating: 2 methods
 - RTL code explicitly specifies clock gating
 - Clock gating cell explicitly instantiated in RTL

• Conventional RTL Code

```
//always clock the register
always @ (posedge clk) begin
    if (enable) q <= din;
end
```

• Low Power Clock Gated RTL


```
//only clock the ff when enable is true
assign gclk = enable && clk;
always @ (posedge gclk) begin
    q <= din;
end
```

• Instantiated Clock Gating Cell

```
//instantiate a clock gating cell
clkgx1 i1 (.en(enable), .cp(clk), .gclk_out(gclk));
always @ (posedge gclk) begin
    q <= din;
end
```


CLOCK GATING – GLITCH PROBLEM

 - What happens if there is a glitch on the enable signal?





Ah, we live in a perfect world! 😊

Not so Fast!

 


CLOCK GATING – GLITCH PROBLEM

 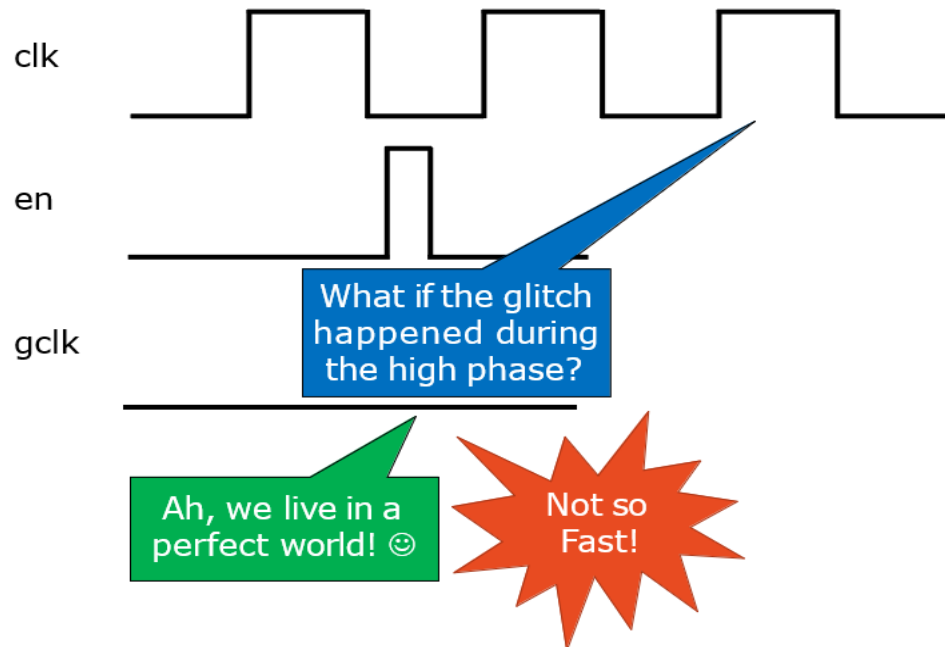- What happens if there is a glitch on the enable signal?



CLOCK GATING – GLITCH PROBLEM

 
- What happens if there is a glitch on the enable signal?



Ah, we live in a perfect world! ☺



Not so Fast!

 Maybe the world aint so perfect after all...



SOLUTION: GLITCH-FREE CLOCK GATE

  
- By latching the enable signal during the positive phase, we can eliminate glitches:



```
//clock gating with glitch prevention latch
always @ (enable or clk)
begin
    if (!clk)
        en_out <= enable;
    end
    assign gclk = en_out && clk;
```

MERGING CLOCK ENABLE GATES

 - Clock gates with common enable can be merged
 - Lower clock tree power, fewer gates
 - May impact enable signal timing and skew.




DATA GATING

- While clock gating is very well understood and automated, a similar situation occurs due to the toggling of data signals that are not used.
- These situations should be recognized and data gated.


BAD:
 
```
assign add_out = A+B;
assign shift_out = A<<B;
assign out = shift_add ? shift_out : add_out;
```



BETTER:
 
```
assign shift_in_A = A && shift_add;
assign shift_in_B = B && shift_add;
assign shift_out = shift_in_A << shift_in_B;
```



Thank you!