



EE 431: COMPUTER-AIDED DESIGN OF VLSI DEVICES

Memory Design

Nishith N. Chakraborty

November, 2024


DATA DRIVEN WORLD!

  

MEMORY CLASSIFICATION

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		


MEMORY ARCHITECTURE: DECODERS

 


Intuitive architecture for $N \times M$ memory
Too many select signals:
 N words == N select signals

Decoder reduces the number of select signals
 $K = \log_2 N$

ARRAY-STRUCTURED MEMORY ARCHITECTURE

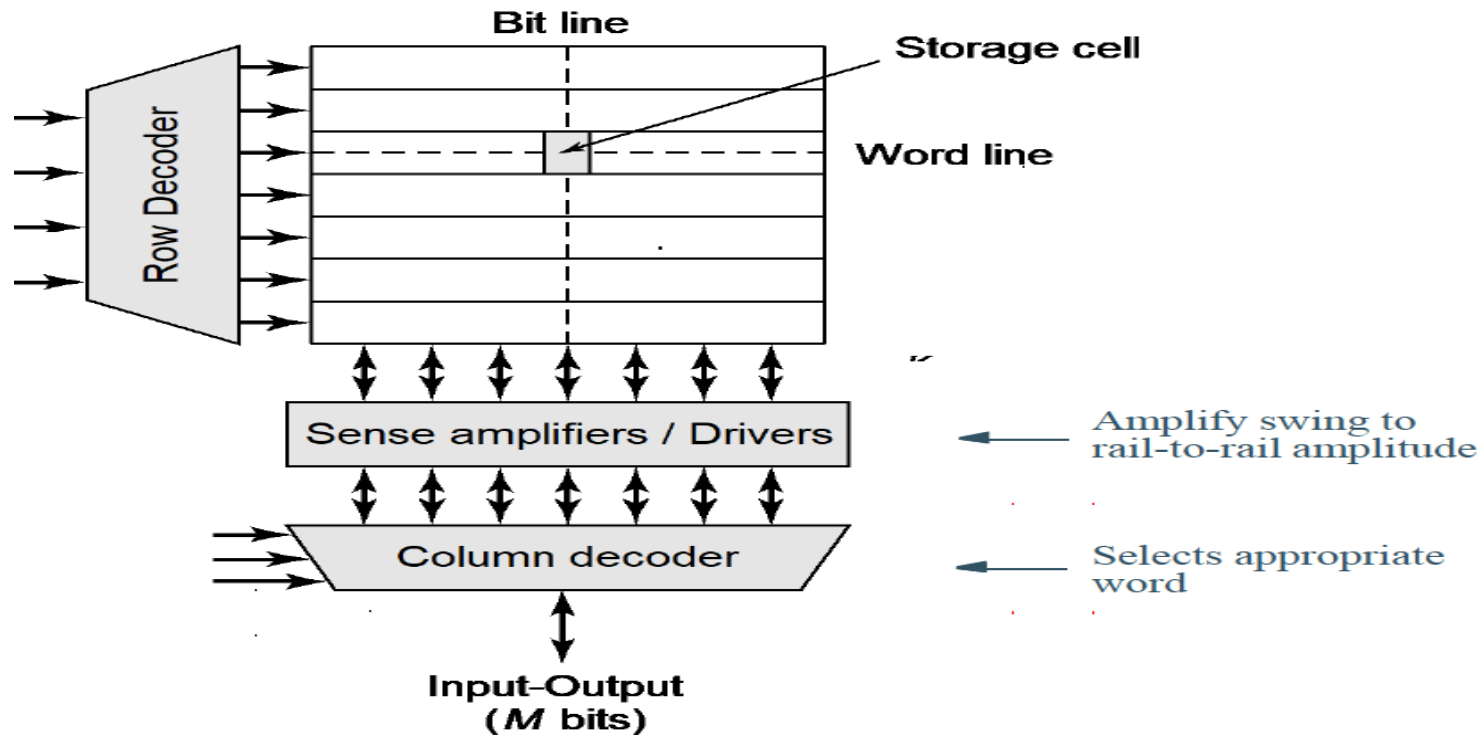

HIERARCHICAL MEMORY ARCHITECTURE

 

Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

READ-WRITE MEMORIES


❑ STATIC (SRAM)

Data stored as long as supply is applied
Large (6 transistors/cell)
Fast
Differential

❑ DYNAMIC (DRAM)

Periodic refresh required
Small (1-3 transistors/cell)
Slower
Single Ended

1-TRANSISTOR DRAM CELL

 


Read Operation

- BL precharged to $V_{DD}/2$
- WL asserted (M_1 turned ON)
- BL charges if C_S stores '1'
- BL discharges if C_S stores '0'


Write Operation

- BL driven to V_{DD} (for write 1) or 0 (for write 0)
- WL asserted
- C_S is charged to $V_{DD} - V_{THN}$ or discharged to 0


1-TRANSISTOR DRAM CELL

 

- Destructive Read
- Needs Refresh

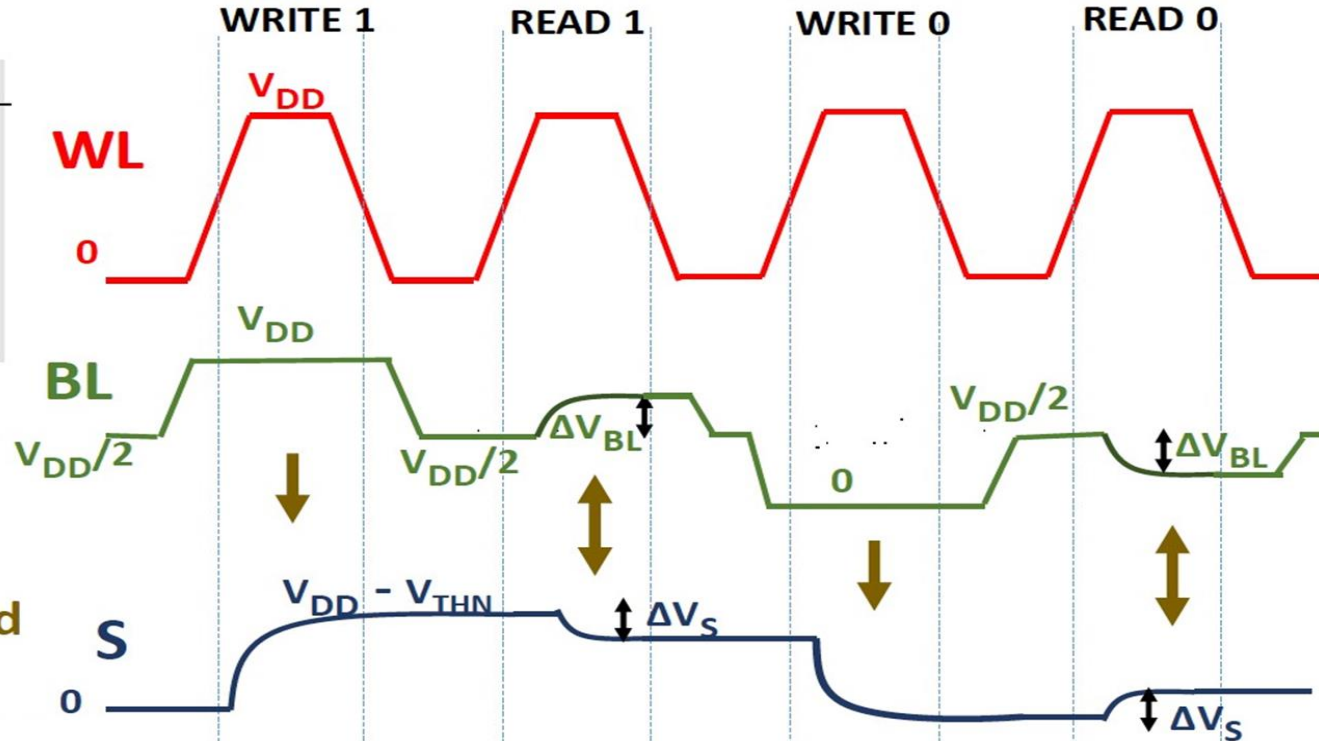


CHARGE SHARING DURING READ

 

$$V_{PRE} = V_{DD}/2$$


$$V_S = 0 \text{ or } V_{DD} - V_{THN}$$

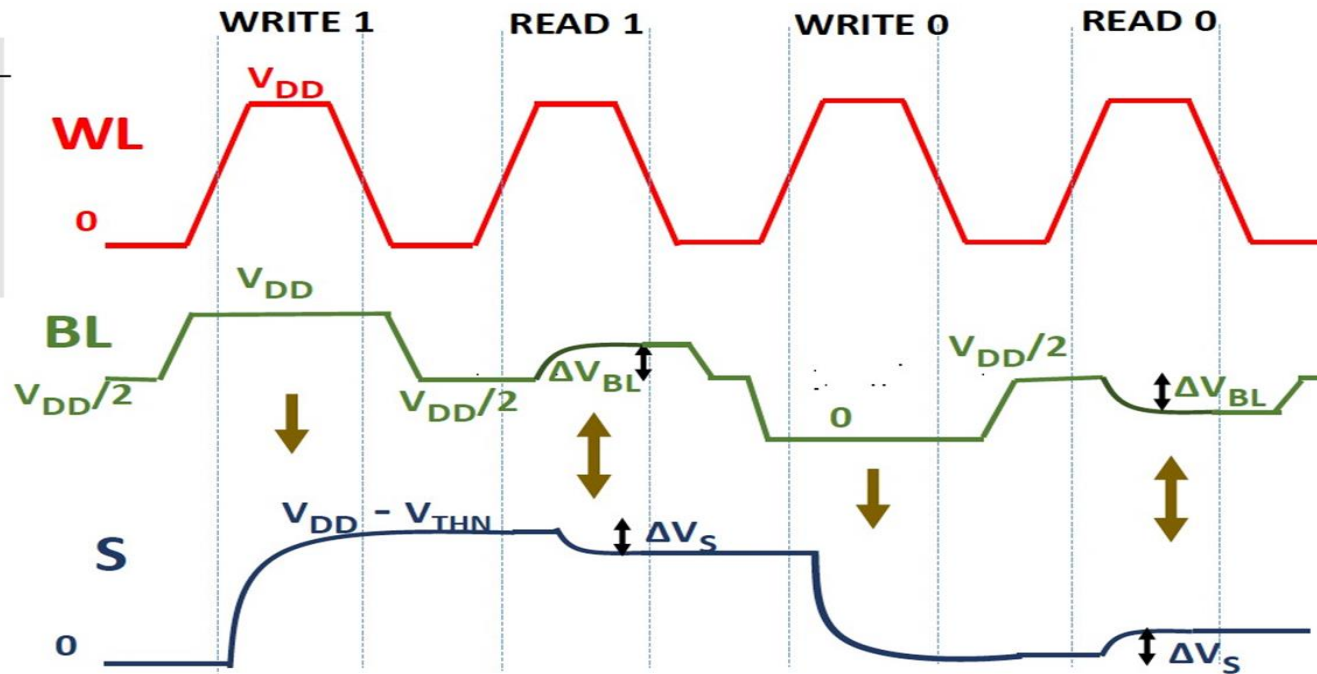


$$\text{Initial } Q = C_S V_S + C_{BL} V_{PRE}$$

$$\text{Final } Q = (C_S + C_{BL}) V_{FINAL}$$

SENSE AMPLIFIER OPERATION

 

3-T DRAM CELL

 


Read Operation

- RBL precharged to V_{DD}
- RWL asserted (M3 turned ON)
- BL remains at V_{DD} if C_S stores '0' (M2 is OFF)
- BL discharges if C_S stores '1' (M2 is ON)


Write Operation

- WBL driven to V_{DD} (for write 1) or 0 (for write 0)
- WWL asserted (M1 turned ON)
- C_S is charged to $V_{DD} - V_{THN}$ or discharged to 0

3-T DRAM CELL


 


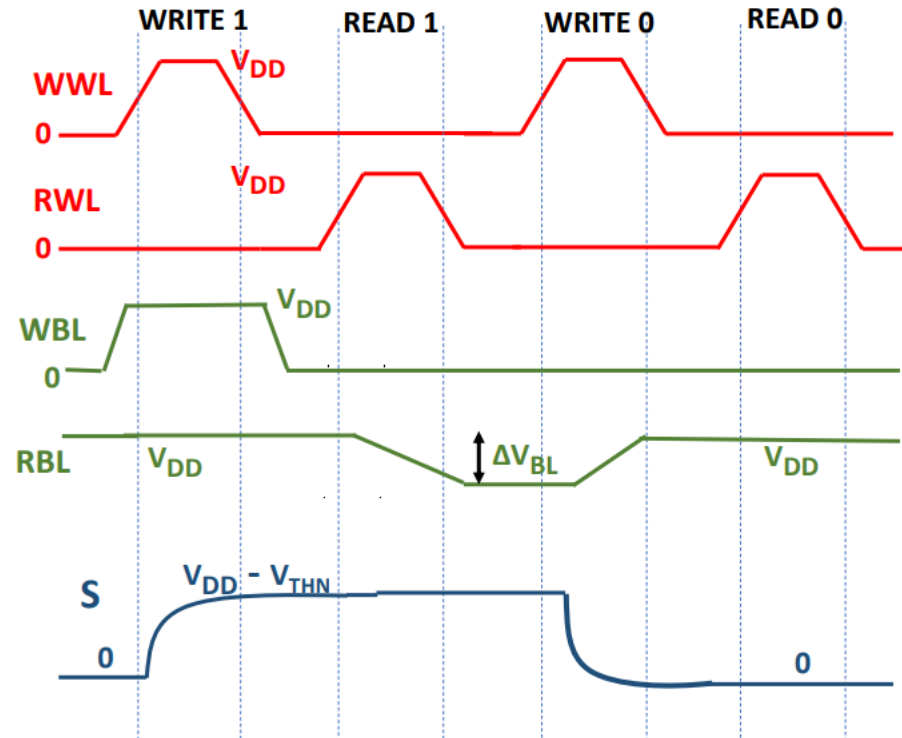- Non-Destructive Read
- No Refresh
- Incomplete swing at S. (WL overdrive solves this issue)




12T SRAM CELL

 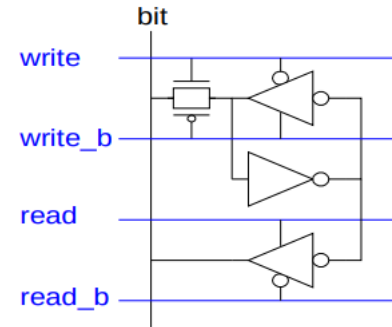- Basic building block: SRAM Cell
 - Holds one bit of information, like a latch
 - Must be read and written
- 12-transistor (12T) SRAM cell
 - Use a simple latch connected to bitline
 - 46 x 75 λ unit cell





6T SRAM CELL

 - Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- Read:
 - Precharge bit, bit_b
 - Raise wordline
- Write:
 - Drive data onto bit, bit_b
 - Raise wordline




SRAM READ

  - Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex: $A = 0, A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- Read stability
 - A must not flip
 - $N1 \gg N2$




SRAM WRITE

 - Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- Writability
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM SIZING

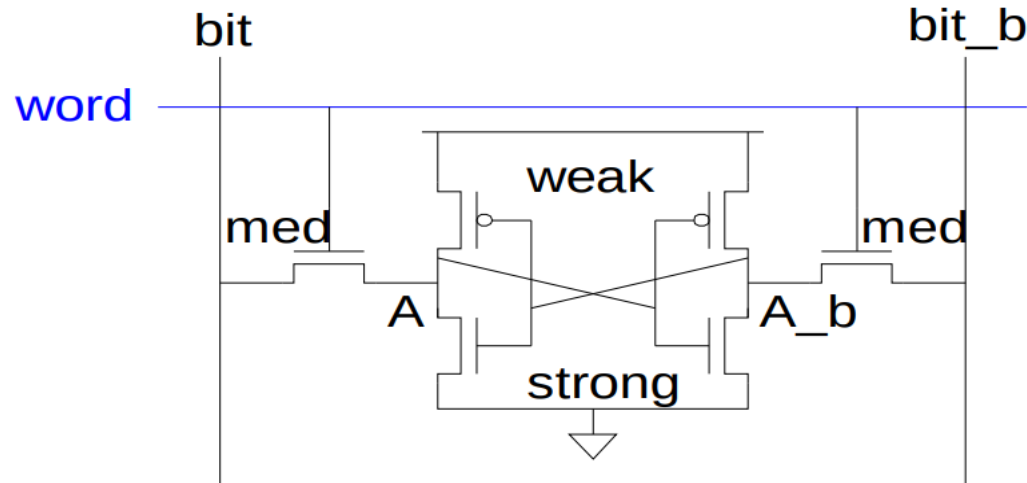- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell




SRAM COLUMN EXAMPLE

Read



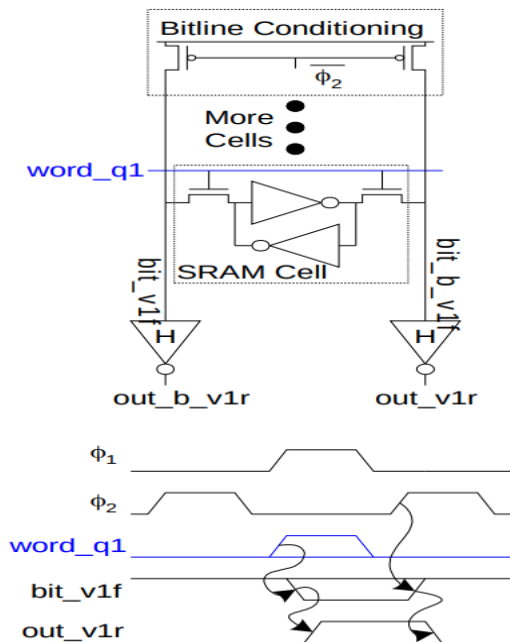


Write

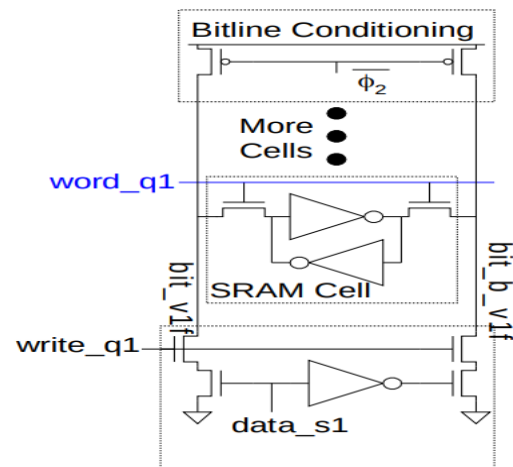

SRAM LAYOUT

 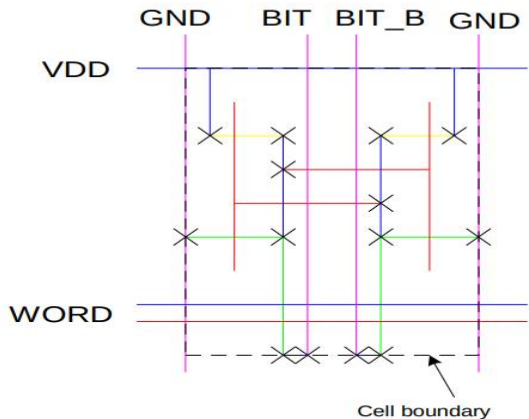
 
- Cell size is critical: $26 \times 45 \lambda$ (even smaller in industry)
- Tile cells sharing VDD, GND, bitline contacts





DECODERS

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

 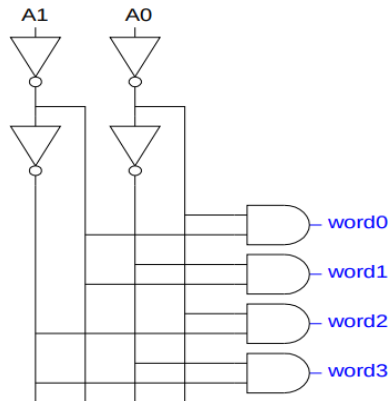


Pseudo-nMOS

  


DECODER LAYOUT

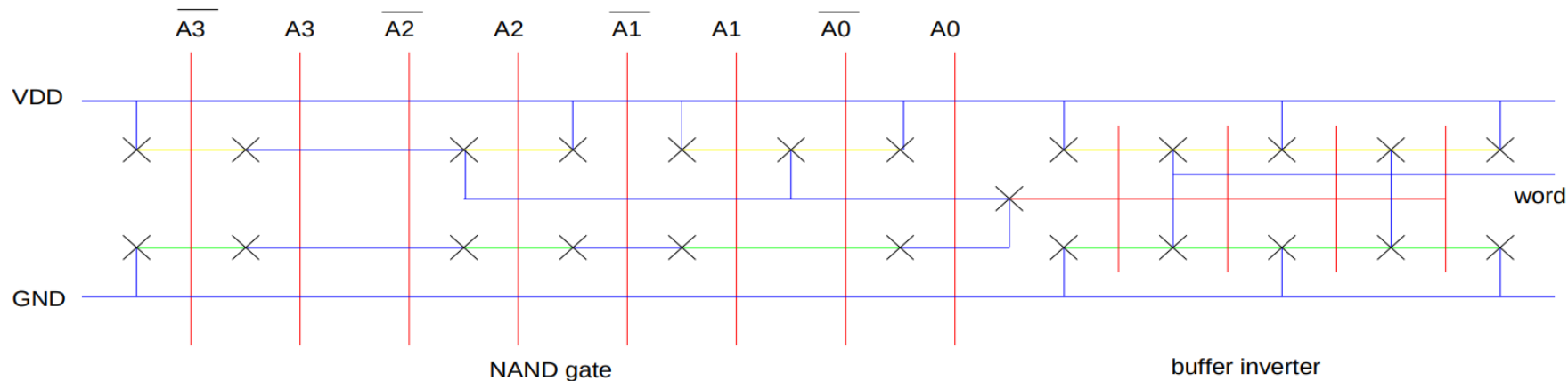- Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




LARGE DECODERS

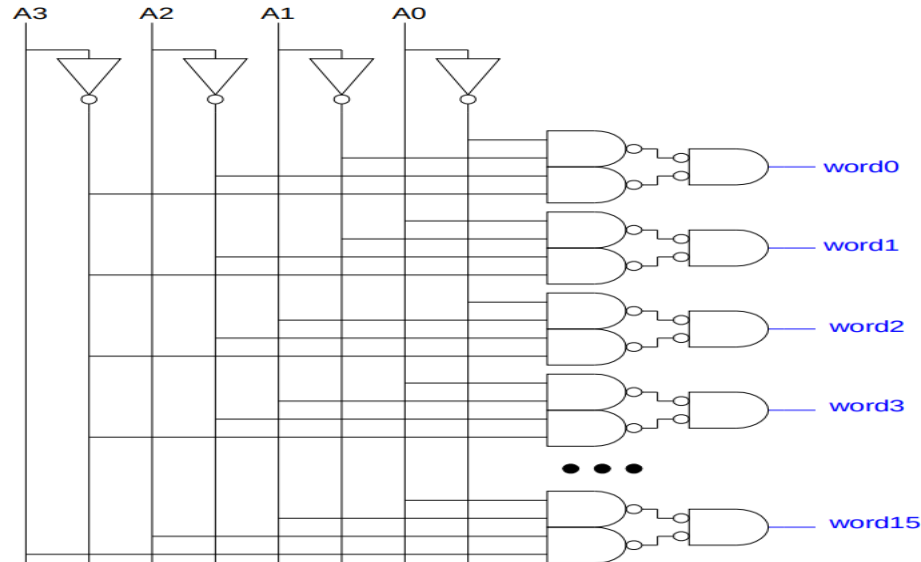- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



PREDECODING

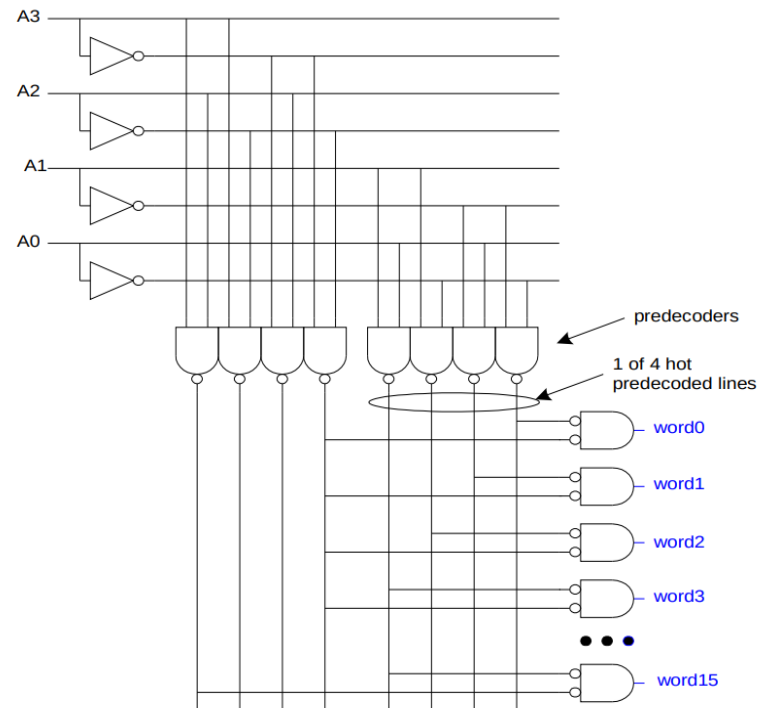- Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort




COLUMN CIRCUITRY


- Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing

BITLINE CONDITIONING

- Precharge bitlines high before reads

 

 - Equalize bitlines to minimize voltage difference when using sense amplifiers




SENSE AMPLIFIERS

- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- $t_{pd} \approx (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce ΔV)


DIFFERENTIAL PAIR AMP

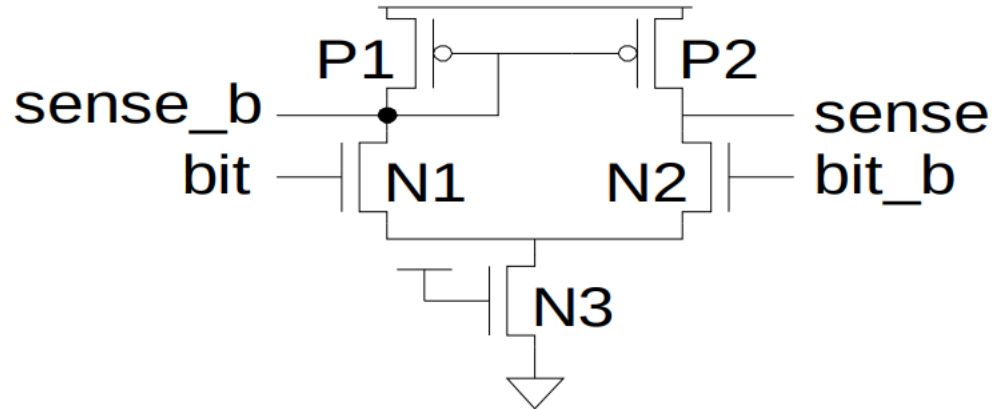- Differential pair requires no clock
- But always dissipates static power




CLOCKED SENSE AMP

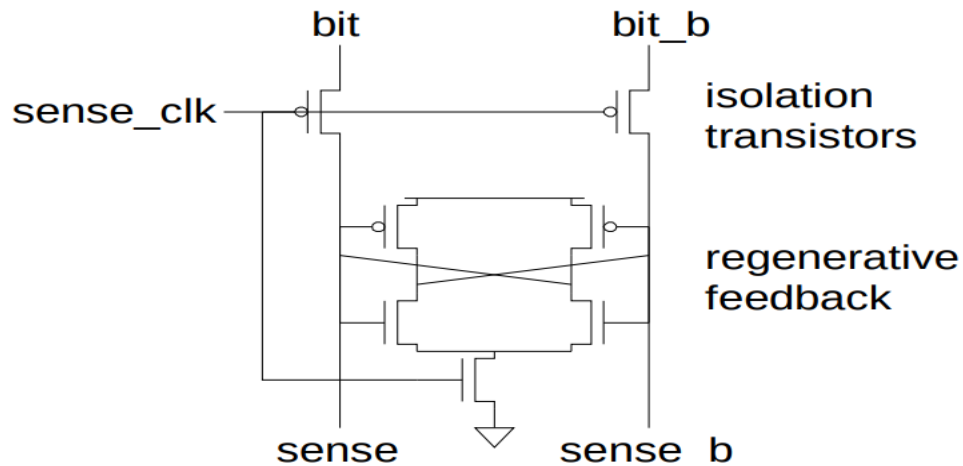- Clocked sense amp saves power
- Requires sense_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance




COLUMN MULTIPLEXING: TREE DECODER MUX

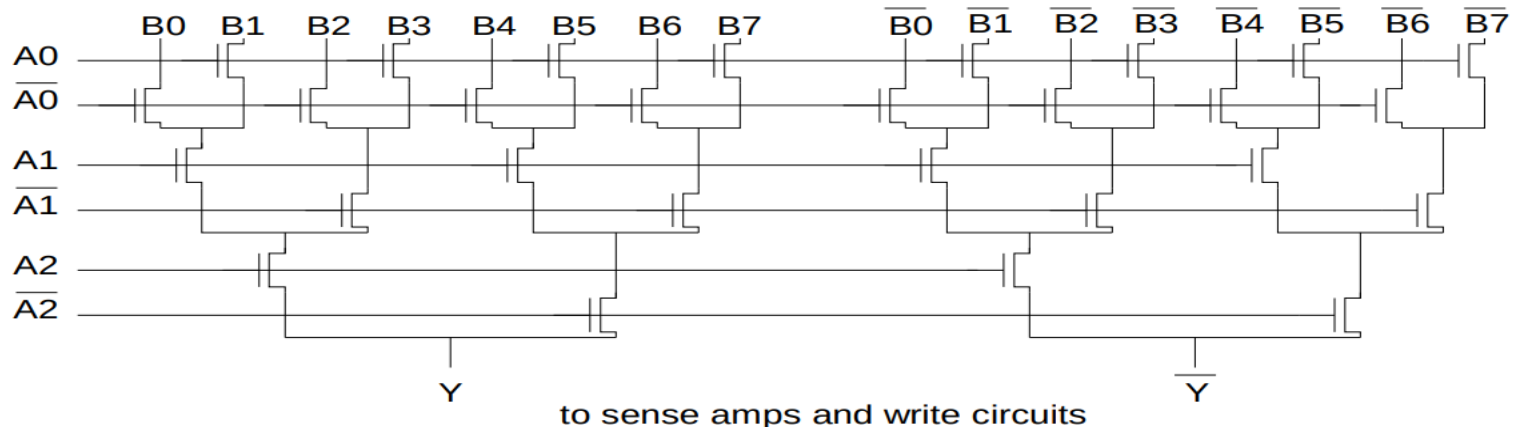- Column MUX can use pass transistors
 - Use NMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ MUX
 - No external decoder logic needed




SINGLE PASS-GATE MUX

 - Or eliminate series transistors with separate decoder




OTHER SRAM BIT-CELLS

 


5T

I. Calson et. al., ESSCIRC05

 


6T

 


7T

K. Takeda et. al., ISSCC05

 

8T (Register File)

L. Chang et. al., VLSI Tech.'05

 






10T

B. Calhoun et. al., ISSCC06


- 5T, 8T, 10T cells - single ended.
- 8T/10T decoupled read and write operation.
- No in-built process variation tolerance

VARIABILITY: SOURCES & AN EXAMPLE

     - Line Edge Roughness
- Random Dopant Fluctuations
- Non-uniform Temperature




 12 identical ring oscillators placed across 250 mm² chip







IMPACT OF PARAMETER VARIATION



Random Dopant Fluctuation

 
    
$$\delta V_t = \Delta V_{t-GLOBAL} + \delta V_{t-LOCAL}$$




INTER-DIE VARIATION & CELL FAILURES

  

Low-Vt Corners



- Read failure ↑
- Hold failure ↑

 

High-Vt Corners

- Access failure ↑
- Write failure ↑


IDENTIFYING THE VT CORNERS

  



Monitor circuit parameters, e.g. leakage current

Effect of inter-die variation can be masked by intra-die variation


SELF-REPAIR TECHNIQUE

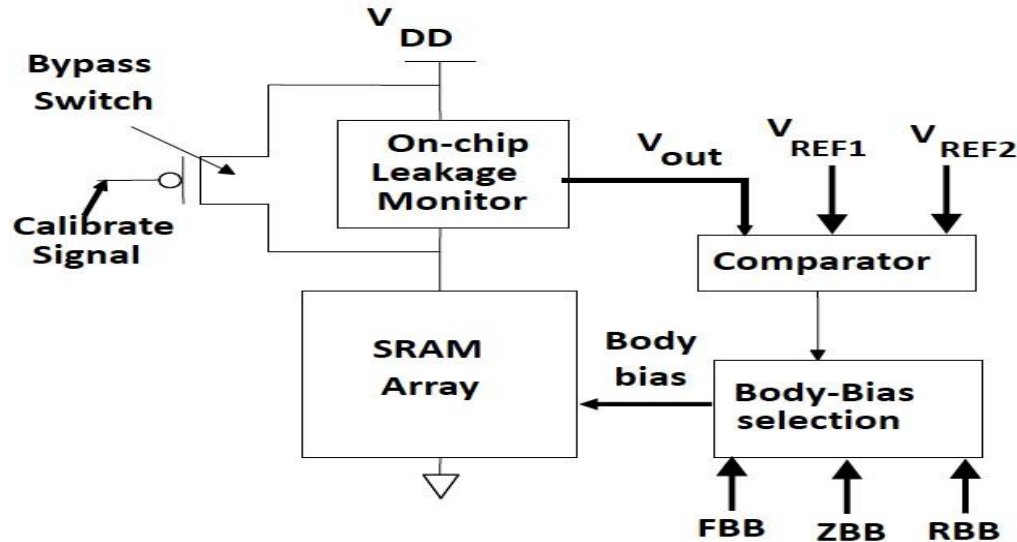

  
Entire array leakage is monitored to detect inter-die corner and proper body-bias is selected




NON-VOLATILE MEMORY TECHNOLOGIES

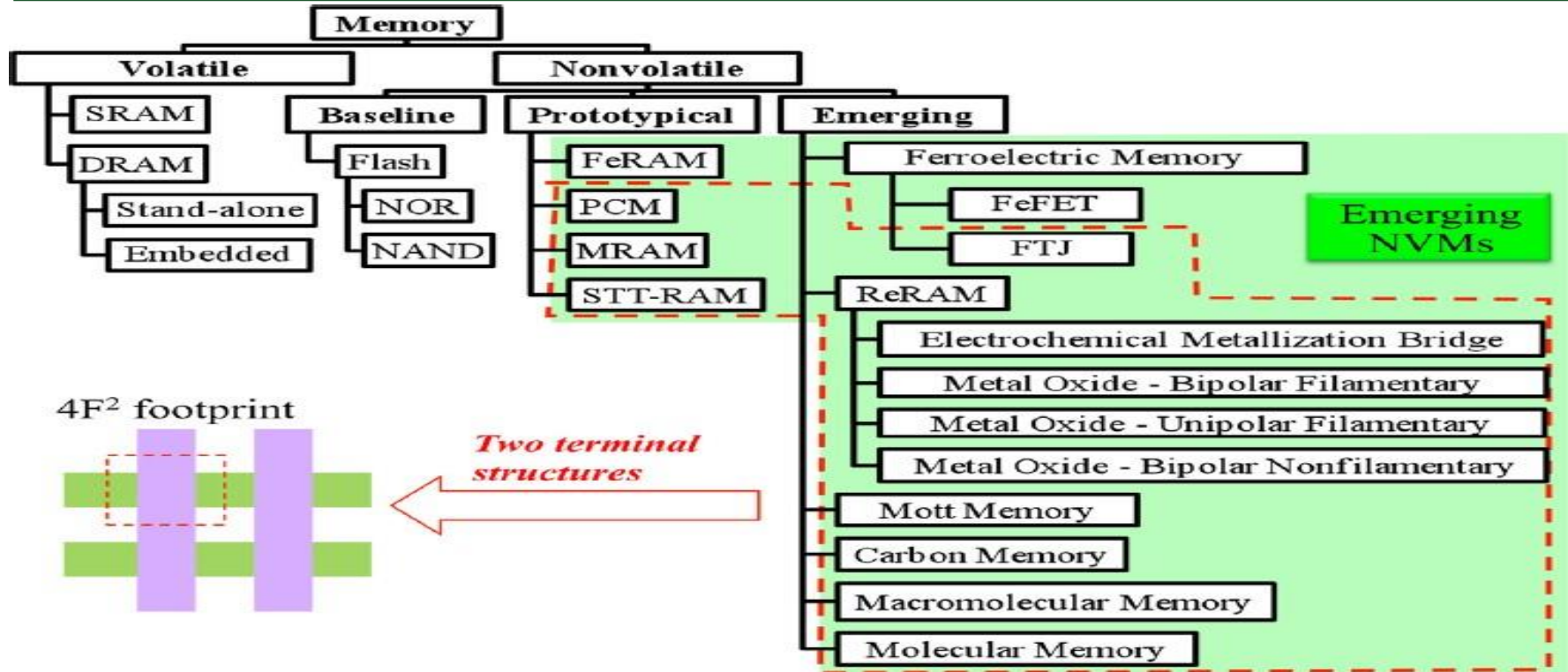

NON-VOLATILE MEMORY TECHNOLOGIES

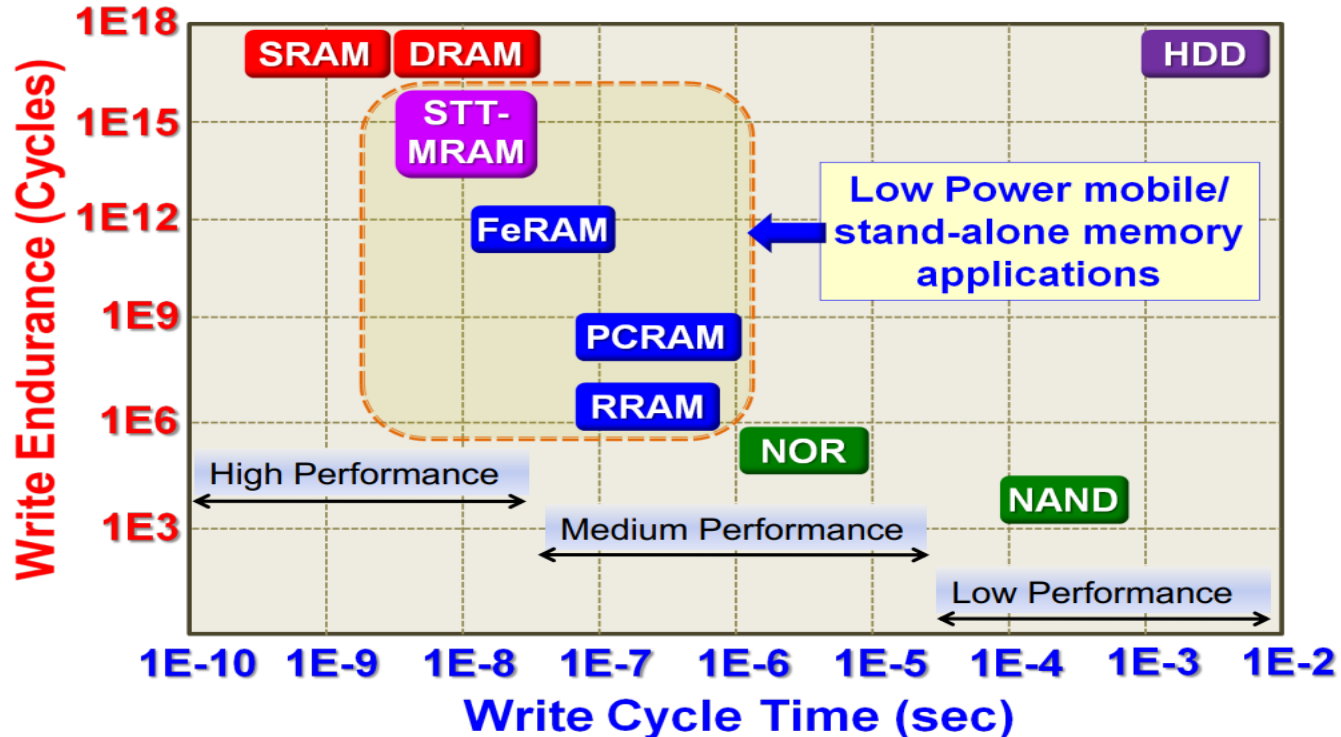

RESISTIVE RAM (RRAM)

 

N. Shukla, R. K. Ghosh, B. Grisafe and S. Datta, "Fundamental mechanism behind volatile and non-volatile switching in metallic conducting bridge RAM," *2017 IEEE International Electron Devices Meeting (IEDM)*, 2017.

RESISTIVE RAM (RRAM): EVALUATION



Positive Features

- High ON-OFF ratio
- Highly scalable
- CMOS compatibility

Limitations

- Limited endurance
- Variations
- Low retention time
(in case of thin filament)

PHASE CHANGE RAM (PCRAM)

  

- Usually made of 'GeSbTe', or in short GST
- Changes the crystal structure from amorphous to crystalline (and vice versa) to switch resistive states

S. Yu and P. Chen, "Emerging Memory Technologies: Recent Trends and Prospects," in *IEEE Solid-State Circuits Magazine*, vol. 8, no. 2, pp. 43-56, Spring 2016.

PHASE CHANGE RAM (PCRAM): EVALUATION

Positive Features

- High ON-OFF ratio
- High retention
- Multilevel possible
- CMOS compatible

Limitations

- High switching energy
- Slow transitions
- Resistance drift → Low retention
(due to relaxation of amorphous phase)


S. Yu and P. Chen, "Emerging Memory Technologies: Recent Trends and Prospects," in *IEEE Solid-State Circuits Magazine*, vol. 8, no. 2, pp. 43-56, Spring 2016.

MEMORY BENCHMARK


	MAINSTREAM MEMORIES				EMERGING MEMORIES		
	SRAM	DRAM	FLASH		STT-MRAM	PCRAM	RRAM
			NOR	NAND			
Cell area	$>100 F^2$	$6 F^2$	$10 F^2$	$<4F^2$ (3D)	$6\sim50F^2$	$4\sim30F^2$	$4\sim12F^2$
Multibit	1	1	2	3	1	2	2
Voltage	$<1 V$	$<1 V$	$>10 V$	$>10 V$	$<1.5 V$	$<3 V$	$<3 V$
Read time	$\sim 1 \text{ ns}$	$\sim 10 \text{ ns}$	$\sim 50 \text{ ns}$	$\sim 10 \mu\text{s}$	$<10 \text{ ns}$	$<10 \text{ ns}$	$<10 \text{ ns}$
Write time	$\sim 1 \text{ ns}$	$\sim 10 \text{ ns}$	$10 \mu\text{s} - 1 \text{ ms}$	$100 \mu\text{s} - 1 \text{ ms}$	$<10 \text{ ns}$	$\sim 50 \text{ ns}$	$<10 \text{ ns}$
Retention	N/A	$\sim 64 \text{ ms}$	$>10 \text{ y}$	$>10 \text{ y}$	$>10 \text{ y}$	$>10 \text{ y}$	$>10 \text{ y}$
Endurance	$>1E16$	$>1E16$	$>1E5$	$>1E4$	$>1E15$	$>1E9$	$>1E6 - 1E12$
Write energy (J/bit)	$\sim \text{fJ}$	$\sim 10 \text{ fJ}$	$\sim 100 \text{ pJ}$	$\sim 10 \text{ fJ}$	$\sim 0.1 \text{ pJ}$	$\sim 10 \text{ pJ}$	$\sim 0.1 \text{ pJ}$
Notes: F: feature size of the lithography. The energy estimation is on the cell-level (not on the array-level). PCRAM and RRAM can achieve less than $4F^2$ through 3D integration. The numbers of this table are representative (not the best or the worst cases).							

S. Yu and P. Chen, "Emerging Memory Technologies: Recent Trends and Prospects," in *IEEE Solid-State Circuits Magazine*, vol. 8, no. 2, pp. 43-56, Spring 2016.




STANDARD STT MRAM

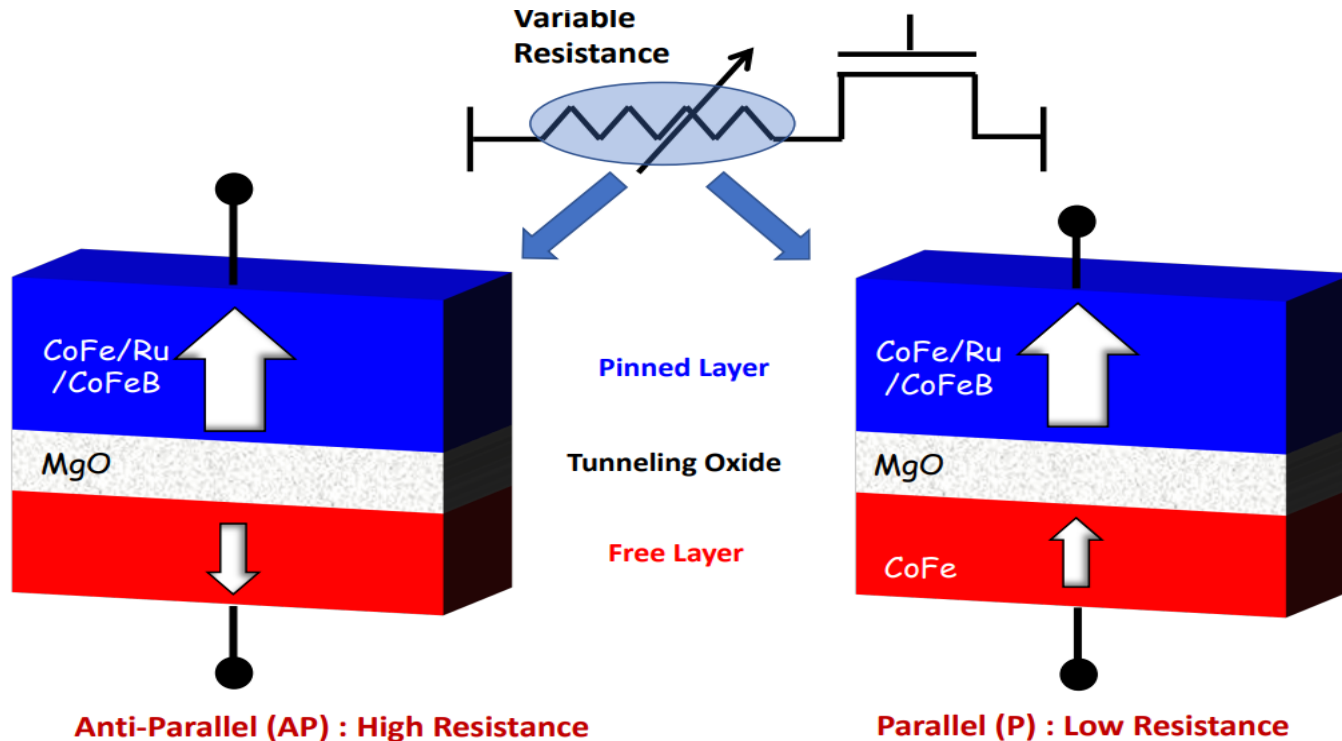

STANDARD STT MRAM: CURRENT BASED WRITE

 

SPIN BASED MEMORY

   

Thank you!